

AN-31 amplifier circuit collection

ABSTRACT

This application report provides basic circuits of the Texas Instruments amplifier collection.

Contents

1	Basic Circuits	3
2	Signal Generation	15
3	Signal Processing	24
4	References	41

List of Figures


1	Inverting Amplifier.....	3
2	Non-Inverting Amplifier.....	3
3	Difference Amplifier.....	4
4	Low-Power Difference Amplifier	4
5	Inverting Summing Amplifier	5
6	Non-Inverting Summing Amplifier	5
7	Inverting Amplifier With High Input Impedance	6
8	Two-Stage Inverting Amplifier With High Input Impedance	6
9	AC Coupled Non-Inverting Amplifier	7
10	Practical Differentiator.....	7
11	Integrator.....	8
12	Current to Voltage Converter (Transimpedance Amplifier).....	8
13	Reference Voltage Generator	9
14	Neutralizing Input Capacitance to Optimize Response Time	9
15	Threshold Detector for Photodiodes	10
16	Double-Ended Limit Detector	10
17	Multiple Aperture Window Discriminator	11
18	Offset Voltage Adjustment for Inverting Amplifiers	12
19	Offset Voltage Adjustment for Non-Inverting Amplifiers.....	12
20	Offset Voltage Adjustment for Voltage Followers	13
21	Offset Voltage Adjustment for Difference Amplifiers.....	13
22	Offset Voltage Adjustment for Inverting Amplifiers With Source Resistance	14
23	Sine Wave Generator With Low Component Count	15
24	Sine Wave Generator.....	15
25	Free-Running Multivibrator.....	16
26	Function Generator	16
27	Pulse Width Modulator	17
28	Improved Howland Current Pump	18
29	Wien Bridge Oscillator With Automatic Gain Control.....	18
30	Positive Output Voltage Reference	19

31	Buffered Positive Voltage Reference	19
32	Negative Output Voltage Reference	20
33	Buffered Negative Voltage Reference	20
34	Current Sink	21
35	Current Source	21
36	Voltage-to-Current Converter With BJT Output	22
37	Voltage-to-Current Converter With Darlington Pair Output	22
38	Voltage-to-Current Converter With MOSFET Output	23
39	Instrumentation Amplifier	24
40	Variable Gain Instrumentation Amplifier	25
41	Instrumentation Amplifier With ± 100 -V Common Mode Range	26
42	Instrumentation Amplifier With ± 10 -V Common Mode Range	26
43	High Input Impedance Instrumentation Amplifier	27
44	Bridge Amplifier With Temperature Sensitivity	27
45	Precision Diode	27
46	Precision Clamp	28
47	Fast Half Wave Rectifier	28
48	AC to DC Converter	29
49	Peak Detector	29
50	Absolute Value Amplifier	30
51	Sample and Hold I	30
52	Sample and Hold II	31
53	Adjustable Q Notch Filter	31
54	Easily Tuned Notch Filter	32
55	Sallen-Key Two-Stage Bandpass Filter	32
56	Two-Stage Capacitance Multiplier	33
57	Simulated Inductor	33
58	Capacitance Multiplier	34
59	High Pass Sallen-Key Active Filter	34
60	Low Pass Sallen-Key Active Filter	35
61	Current Monitor	35
62	Saturating Servo Preamplifier With Rate Feedback	36
63	Power Booster	36
64	Fast Zero Crossing Detector	37
65	Amplifier for Piezoelectric Transducer	37
66	Temperature Probe	38
67	Photodiode Amplifier I	38
68	Photodiode Amplifier II	39
69	High Input Impedance AC Follower	39
70	Multiplier/Divider	40

Trademarks

All trademarks are the property of their respective owners.

1 Basic Circuits

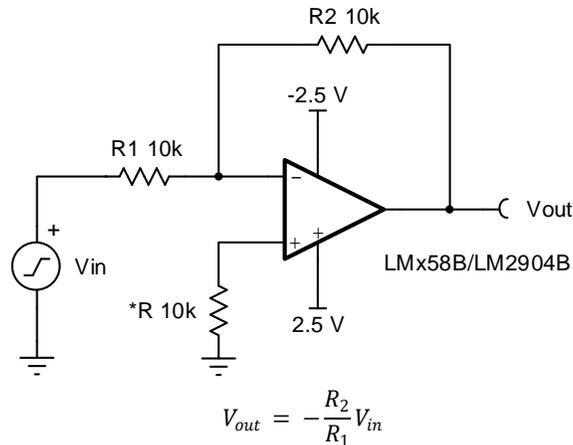

** R Optional to Protect LM358 & LM324*

Devices from Transient Current Spikes

Figure 1. Inverting Amplifier

See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#). To learn more about *R and how to protect LM358/LM2904 devices from transient current spikes at the input, see [23].


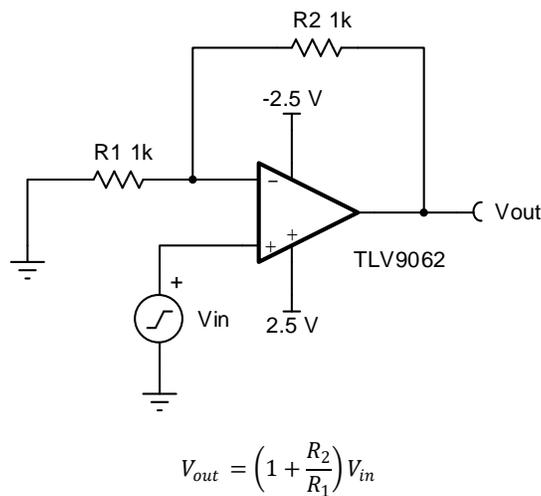


Figure 2. Non-Inverting Amplifier

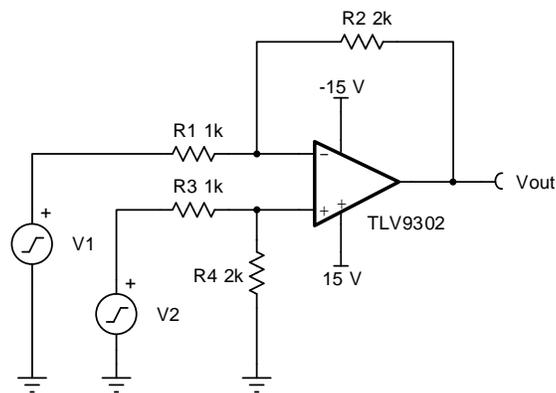See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2}{R_1} V_1$$

$$\text{For } R_1 = R_3 \text{ and } R_2 = R_4$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Figure 3. Difference Amplifier

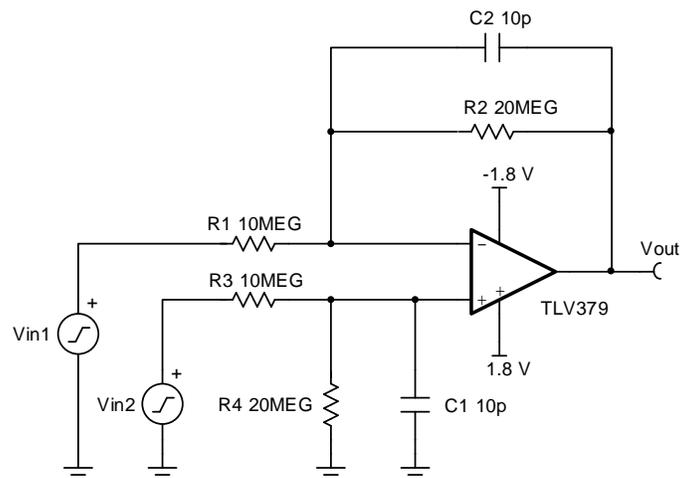See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \left(\frac{R_4}{R_3 + R_4} \right) \left(1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2}{R_1} V_1$$


$$\text{For } R_1 = R_3 \text{ and } R_2 = R_4$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

$$f_{cutoff} = \frac{1}{2\pi C_2 R_2}$$

Figure 4. Low-Power Difference Amplifier

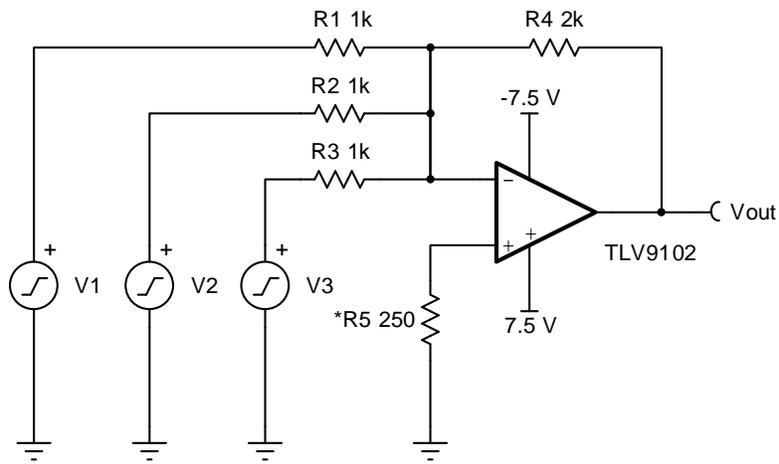See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = -R_4 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

* R₅ Optional for Input Bias Current Cancellation

Figure 5. Inverting Summing Amplifier

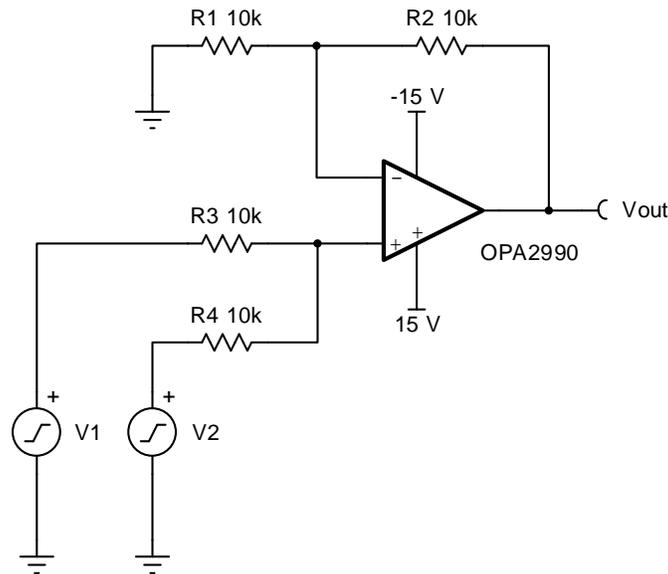See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left(1 + \frac{R_2}{R_1} \right) \left(V_1 \frac{R_4}{R_3 + R_4} + V_2 \frac{R_3}{R_3 + R_4} \right)$$

$$V_{out} = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) (V_1 + V_2) \text{ if } R_3 = R_4$$

Figure 6. Non-Inverting Summing Amplifier

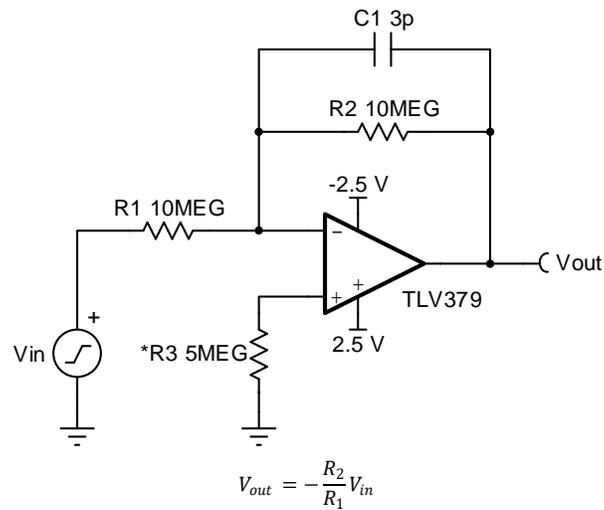See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



* R₃ Optional for Input Bias Current Cancellation

Figure 7. Inverting Amplifier With High Input Impedance

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


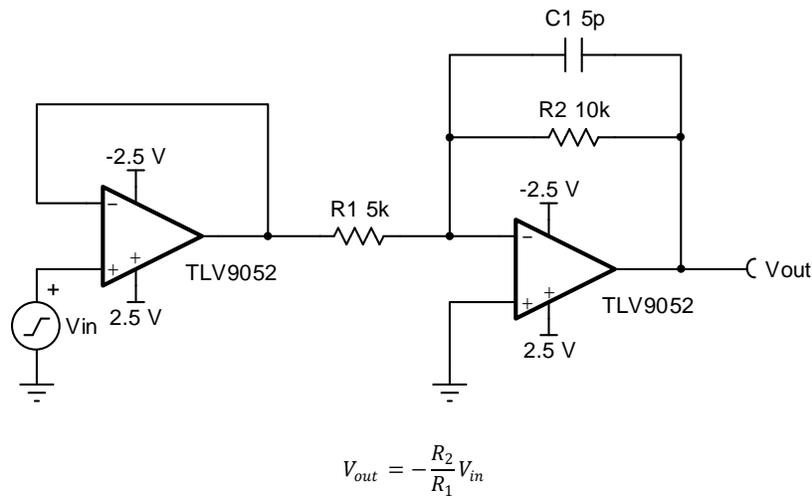


Figure 8. Two-Stage Inverting Amplifier With High Input Impedance

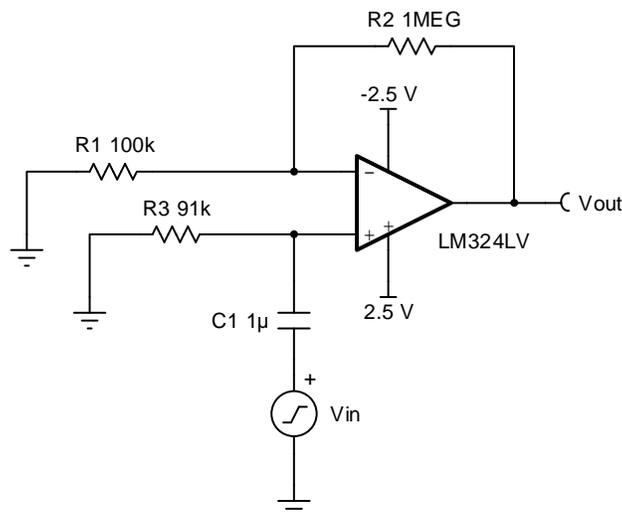Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$R_3 = R_1 || R_2 \text{ for CMRR}$$

$$f_{cutoff\ low} = \frac{1}{2\pi \times C_1 \times R_3}$$

Figure 9. AC Coupled Non-Inverting Amplifier

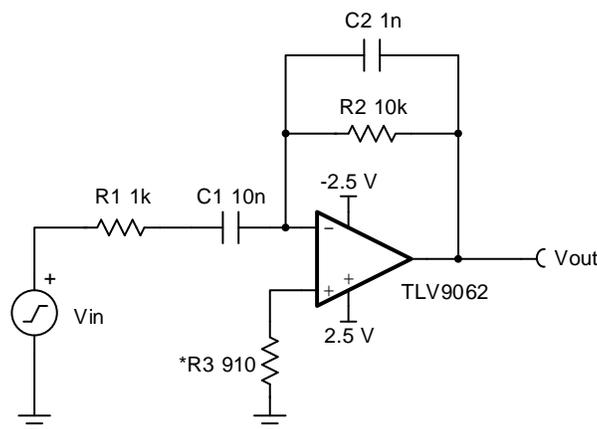See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = -\frac{dV_{in}}{dt}$$

$$f_c = \frac{1}{2\pi R_2 C_1} V_{in}$$


$$f_h = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_2 C_2}$$

$$f_c \ll f_h \ll f_{unity\ gain}$$

* R₃ Optional for Input Bias Current Cancellation

Figure 10. Practical Differentiator

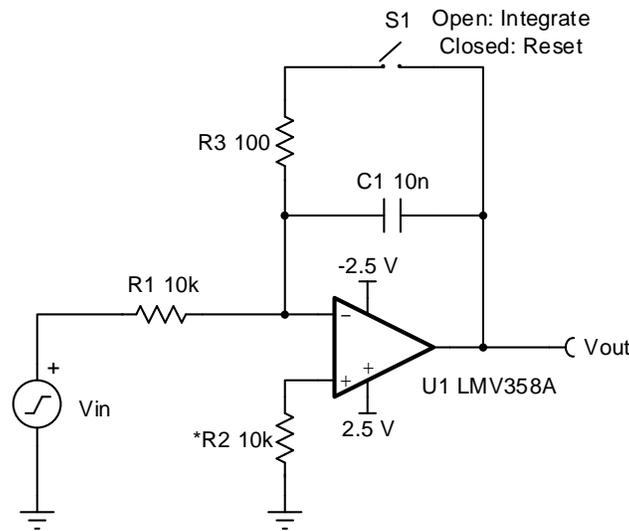See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = -\frac{1}{R_1 C_1} \int_{t_1}^{t_2} V_{in} dt$$


$$f_c = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = R_2$$

* R₂ Optional for Input Bias Current Cancellation

Figure 11. Integrator

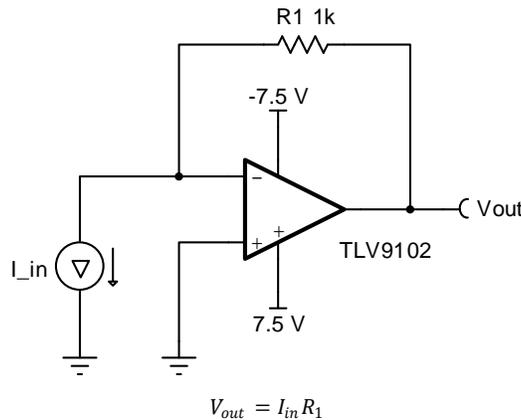See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = I_{in} R_1$$

Figure 12. Current to Voltage Converter (Transimpedance Amplifier)

See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

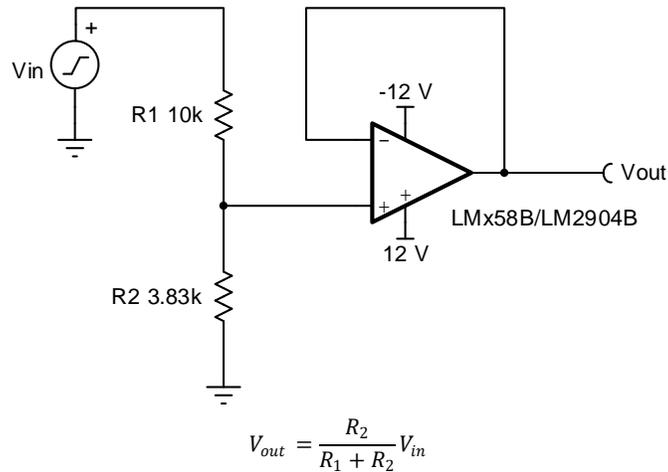


Figure 13. Reference Voltage Generator

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


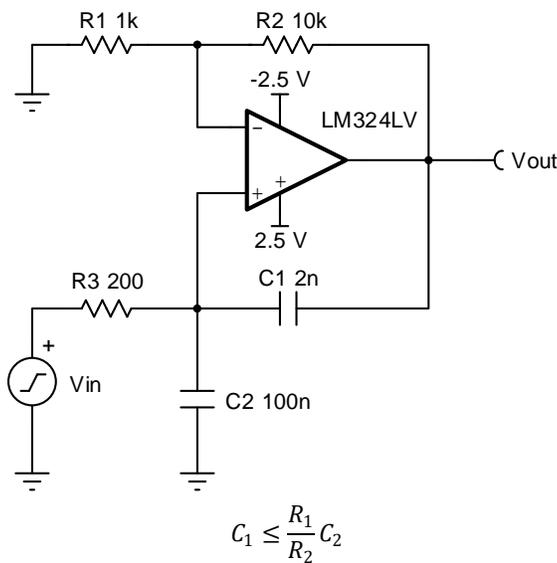


Figure 14. Neutralizing Input Capacitance to Optimize Response Time

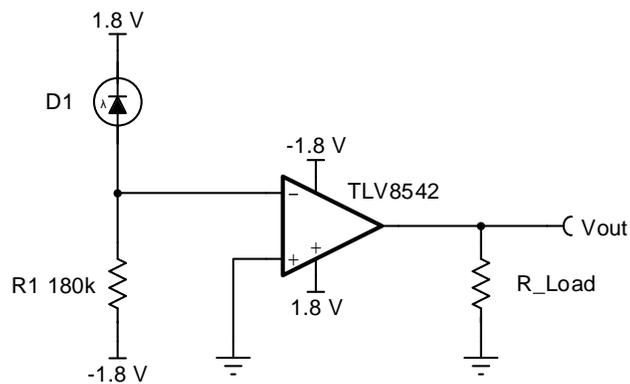Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$V_{out} = 1.8V \Rightarrow$ Diode Off

$V_{out} = -1.8V \Rightarrow$ Diode On

R_1 Controls Sensitivity to Light

Figure 15. Threshold Detector for Photodiodes

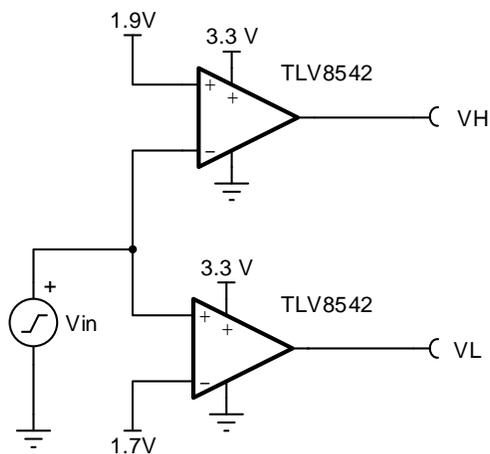For more information on modeling photodiodes, see [8]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




If $V_{in} > 1.9V$, then $V_H = 0$ and $V_L = 3.3V$

If $1.9V > V_{in} > 1.7V$, then $V_H = 3.3V$ and $V_L = 3.3V$

If $V_{in} < 1.7V$, then $V_H = 3.3V$ and $V_L = 0$

Figure 16. Double-Ended Limit Detector

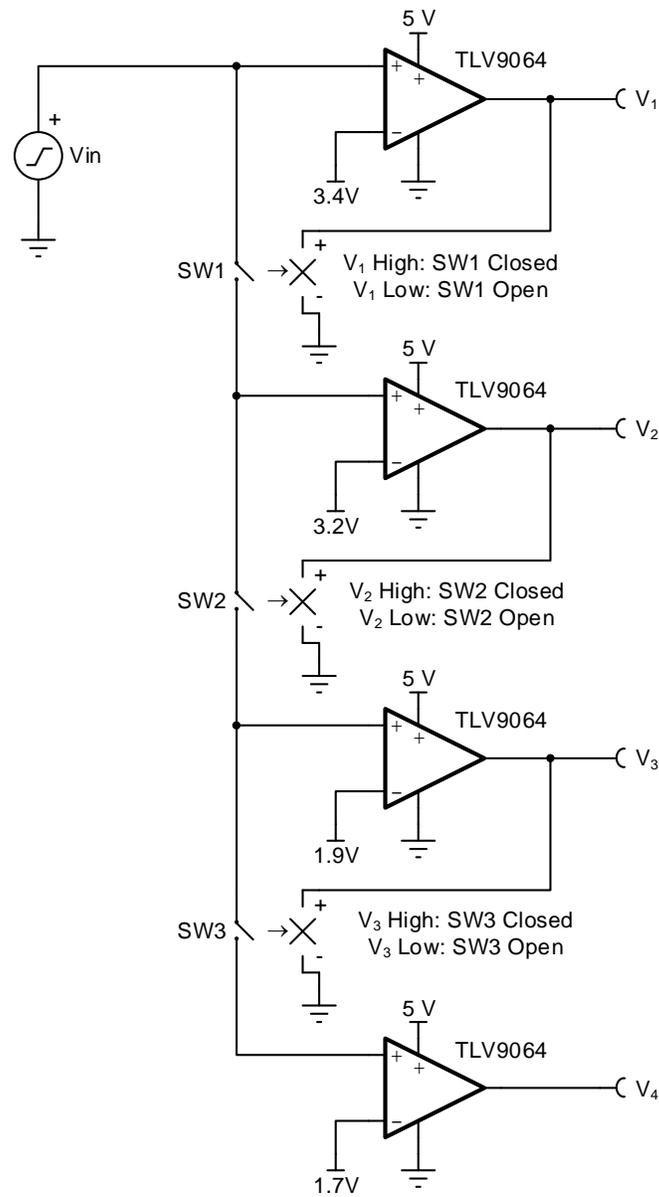
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$\begin{aligned}
 V_{in} > 3.4V &\rightarrow V_1 = 1, V_2 = 1, V_3 = 1, V_4 = 1 \\
 3.4V > V_{in} > 3.2V &\rightarrow V_1 = 0, V_2 = 1, V_3 = 1, V_4 = 1 \\
 3.2V > V_{in} > 1.9V &\rightarrow V_1 = 0, V_2 = 0, V_3 = 1, V_4 = 1 \\
 1.9V > V_{in} > 1.7V &\rightarrow V_1 = 0, V_2 = 0, V_3 = 0, V_4 = 1 \\
 1.7V > V_{in} &\rightarrow V_1 = 0, V_2 = 0, V_3 = 0, V_4 = 0
 \end{aligned}$$

Figure 17. Multiple Aperture Window Discriminator

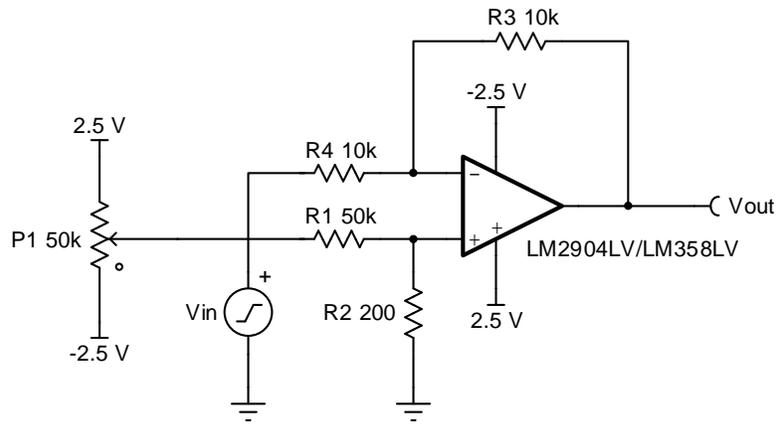Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left(\frac{R_2}{R_1} \right)$$

$$V_{\text{out}} = \left(-\frac{R_3}{R_4} \right) V_{\text{in}}$$

$$R_1 \gg R_2$$

Figure 18. Offset Voltage Adjustment for Inverting Amplifiers

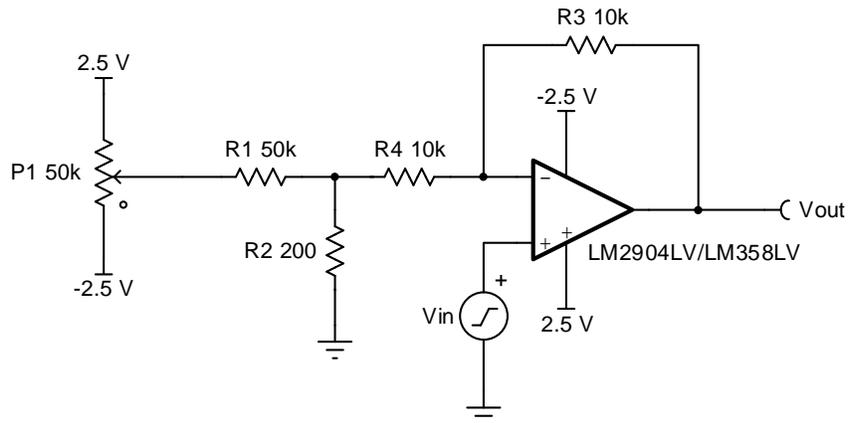Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left(\frac{R_2}{R_1} \right)$$

$$V_{\text{out}} = \left(1 + \frac{R_3}{R_2 + R_4} \right) V_{\text{in}}$$

$$R_1 \gg R_2 \text{ and } R_4 \gg R_2$$

Figure 19. Offset Voltage Adjustment for Non-Inverting Amplifiers

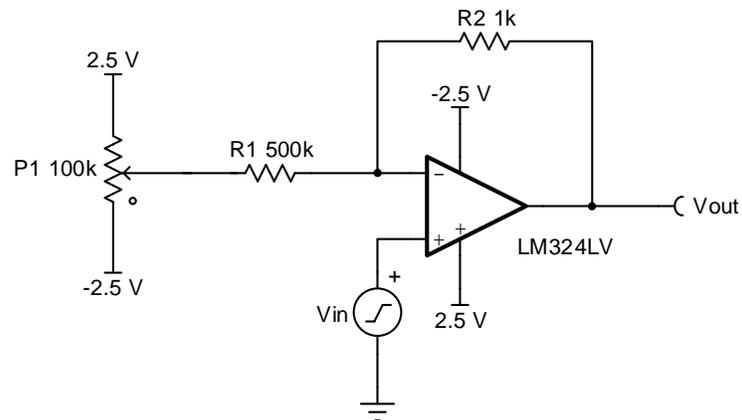Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left(\frac{R_2}{R_1} \right)$$

$$V_{\text{out}} \approx V_{\text{in}}$$

$$R_1 \gg R_2$$

Figure 20. Offset Voltage Adjustment for Voltage Followers

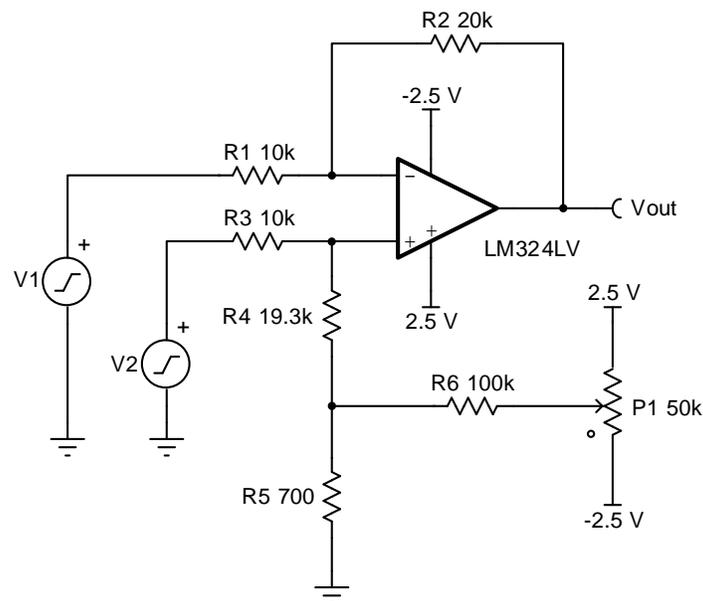Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = R_4 + R_5$$

$$R_1 = R_3$$


$$\text{Offset Range} = V_{\text{supply}} \left(\frac{R_5}{R_5 + R_6} \right) \left(\frac{R_3}{R_3 + R_4} \right)$$

$$V_{\text{out}} = \left(\frac{R_2}{R_1} \right) (V_2 - V_1)$$

$$R_5 \ll \text{Offset Equivalent Resistance}$$

Figure 21. Offset Voltage Adjustment for Difference Amplifiers

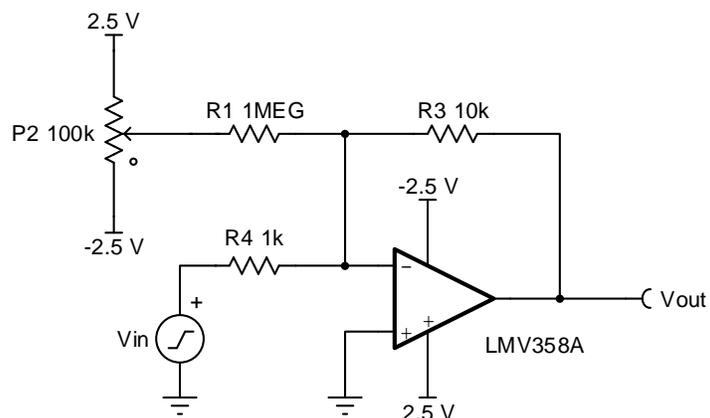Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_3 || R_4 \leq 10k\Omega$$


$$\text{Offset Range} = V_{\text{supply}} \left(\frac{R_3 || R_4}{R_1} \right)$$

$$V_{\text{out}} = \left(-\frac{R_3}{R_4} \right) V_{\text{in}}$$

Figure 22. Offset Voltage Adjustment for Inverting Amplifiers With Source Resistance

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

2 Signal Generation

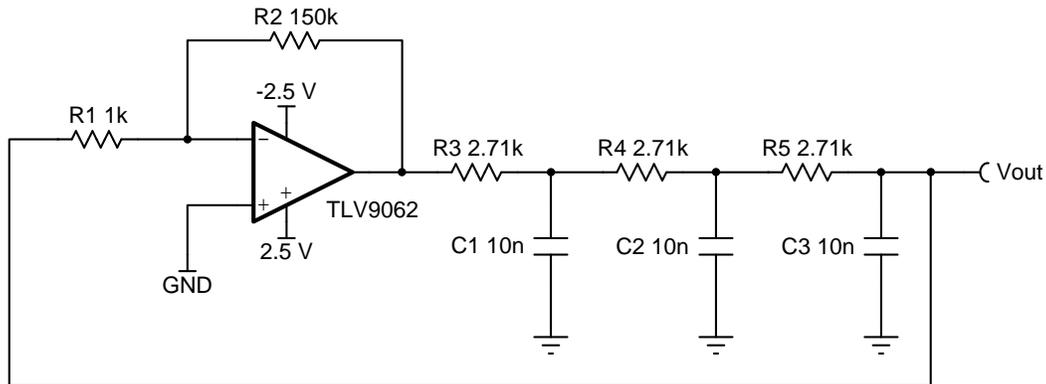


$$\frac{R_2}{R_1} \gg 8$$

Let $R = R_3, R_4, R_5$ and $C = C_1, C_2, C_3$

$$f_{oscillation} \approx \frac{\tan(60^\circ)}{2\pi RC}$$

Figure 23. Sine Wave Generator With Low Component Count

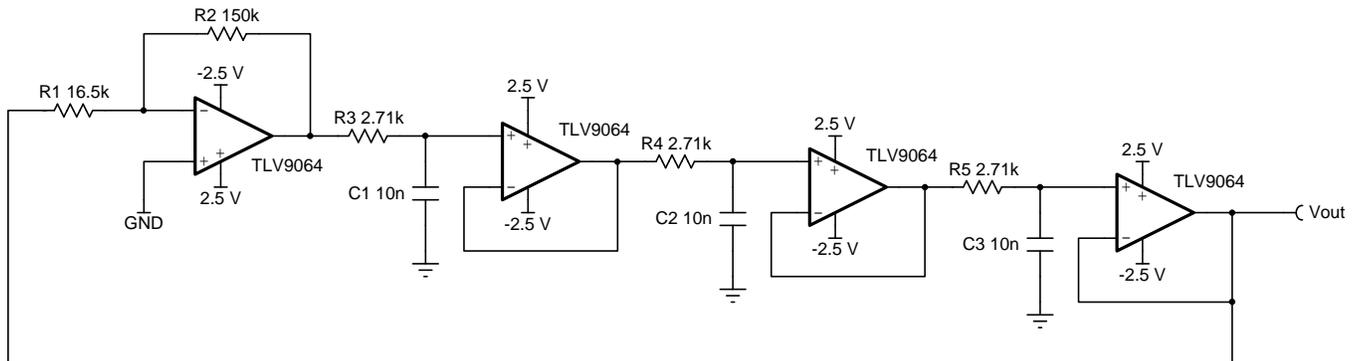For more information on this configuration, also known as a phase-shift oscillator, see [9] and [10]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$8 \leq \frac{R_2}{R_1} \leq 10$$

Let $R = R_3, R_4, R_5$ and $C = C_1, C_2, C_3$

$$f_{oscillation} = \frac{\tan(60^\circ)}{2\pi RC}$$

Figure 24. Sine Wave Generator

For more information on this configuration, also known as a buffered phase-shift oscillator, see [9] and [10]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

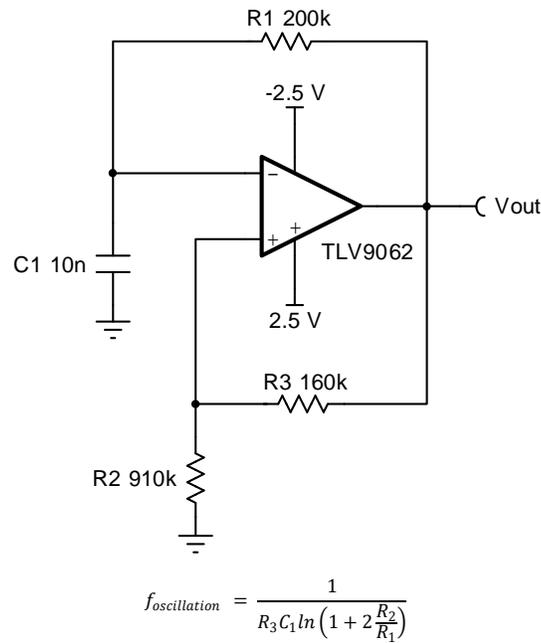


Figure 25. Free-Running Multivibrator

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


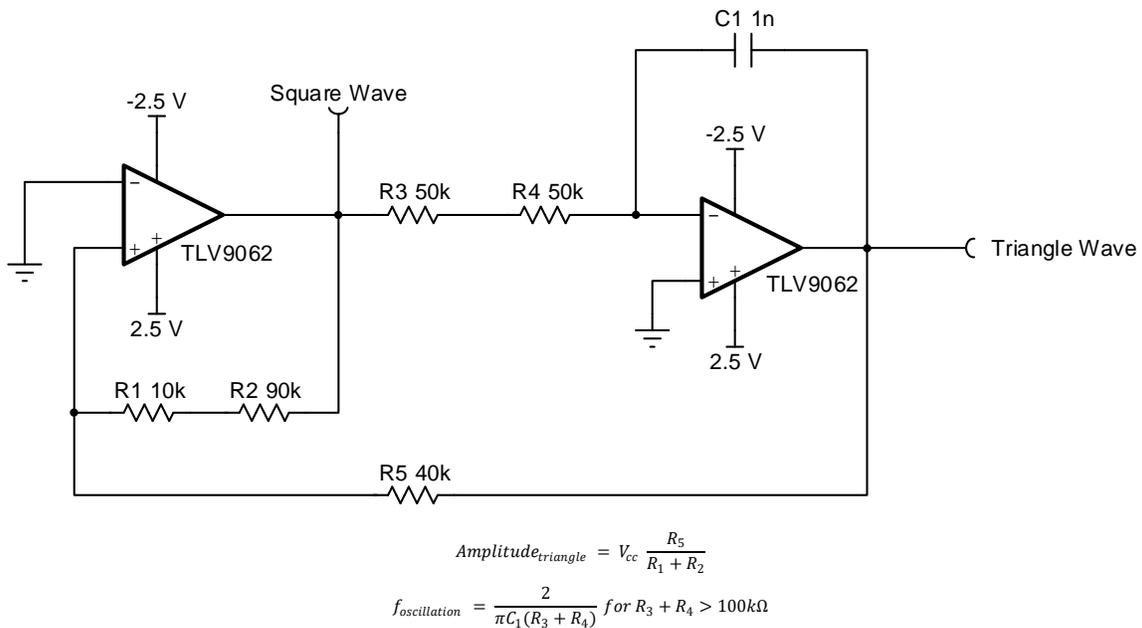


Figure 26. Function Generator

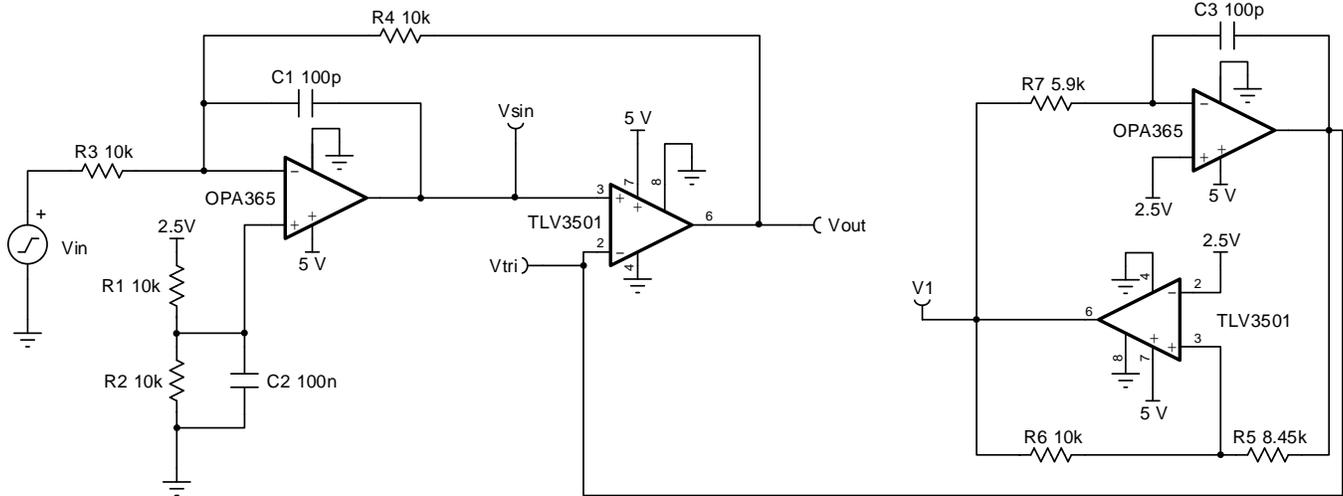See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_1 = R_2 = R_3 = R_4$$

$$V_{tri} > |V_i|$$

$$\frac{R_5}{R_6} = \frac{|V_{tri}|}{|V_1|} \text{ for } V_1 = V_{ref}$$


$$f_{oscillation} = \frac{R_6}{4 \times R_7 \times R_5 \times C_3}$$

$$C_1 > \frac{1}{2\pi \times R_4 \times f_{oscillation}}$$

$$C_2 = \frac{1}{2\pi \times f_{noise\ filter} \times (R_1 || R_2)}$$

Figure 27. Pulse Width Modulator

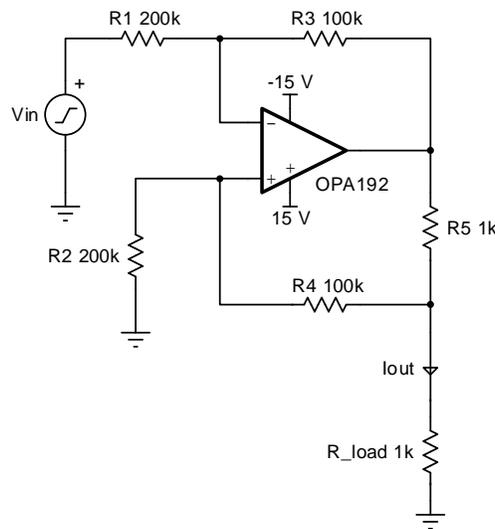See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = -\frac{R_3 V_{in}}{R_1 R_5}$$

$$R_3 = R_4 + R_5$$

$$R_1 = R_2$$

Figure 28. Improved Howland Current Pump

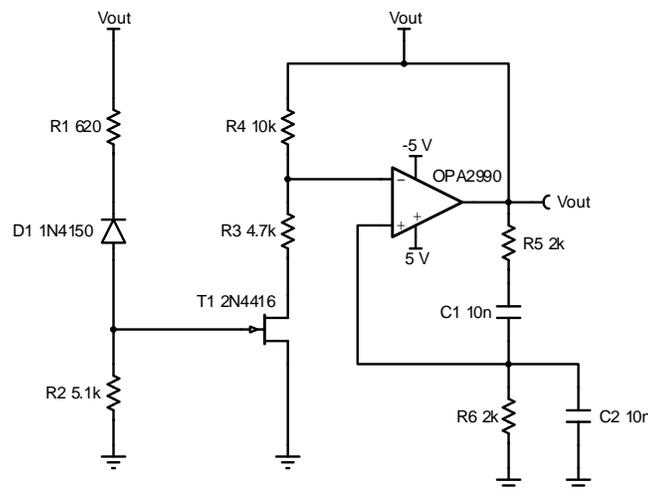For an in-depth dive into this configuration, see our [11]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$f_{oscillation} = \frac{1}{2\pi C_1 R_5}$$

$$\text{Set Gain} = 3.1$$


$$\text{Gain} = \frac{R_3 + R_4}{R_4}$$

$$R_5 = R_6$$

$$C_1 = C_2$$

Figure 29. Wien Bridge Oscillator With Automatic Gain Control

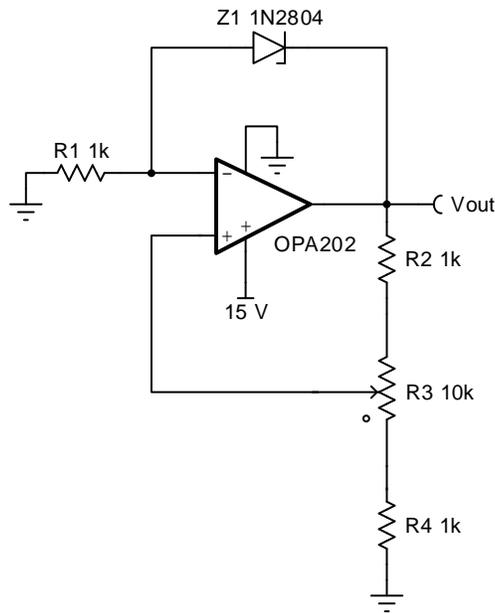Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$7.58V \leq V_{out} \leq 13.93V$$

R_1 controls $V_{out,max}$
 $R_2, R_4,$ & V_{zener} control $V_{out,min}$

Figure 30. Positive Output Voltage Reference

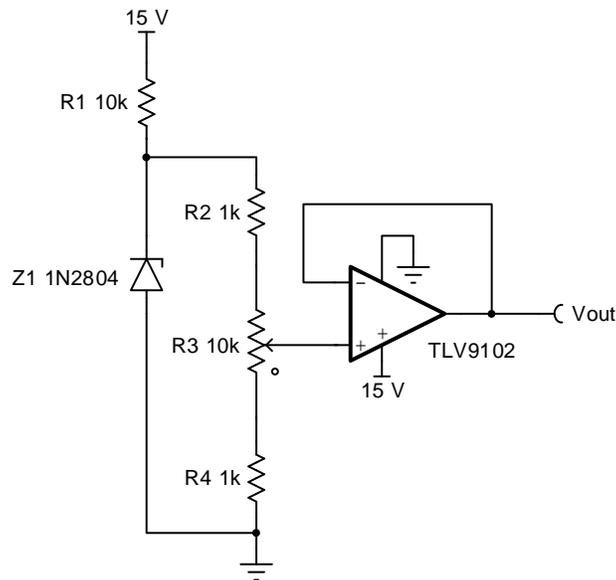See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$500mV \leq V_{out} \leq 5.5V$$

Decreasing R_2 & R_4 increases V_{out} range
 V_{zener} adjusts V_{out} range

Figure 31. Buffered Positive Voltage Reference

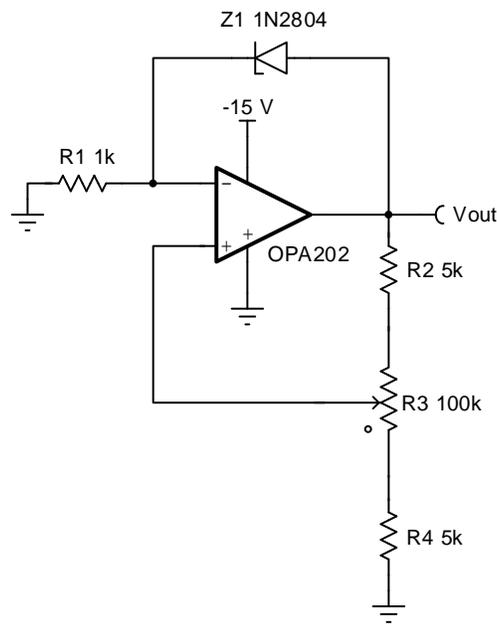See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$-13.9V \leq V_{out} \leq -7.6V$$

Decreasing R_2 and R_4 increases V_{out} range

V_{zener} adjusts V_{out} range

Figure 32. Negative Output Voltage Reference

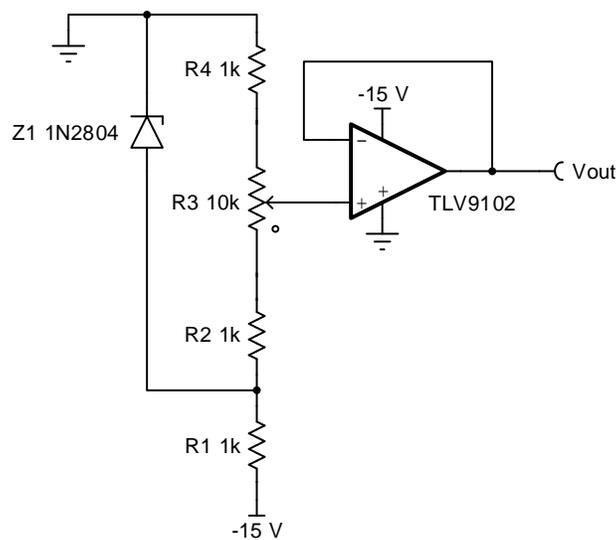See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$-5.5V \leq V_{out} \leq -500mV$$

Decreasing R_2 & R_4 increases V_{out} range

V_{zener} adjusts V_{out} range

Figure 33. Buffered Negative Voltage Reference

See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

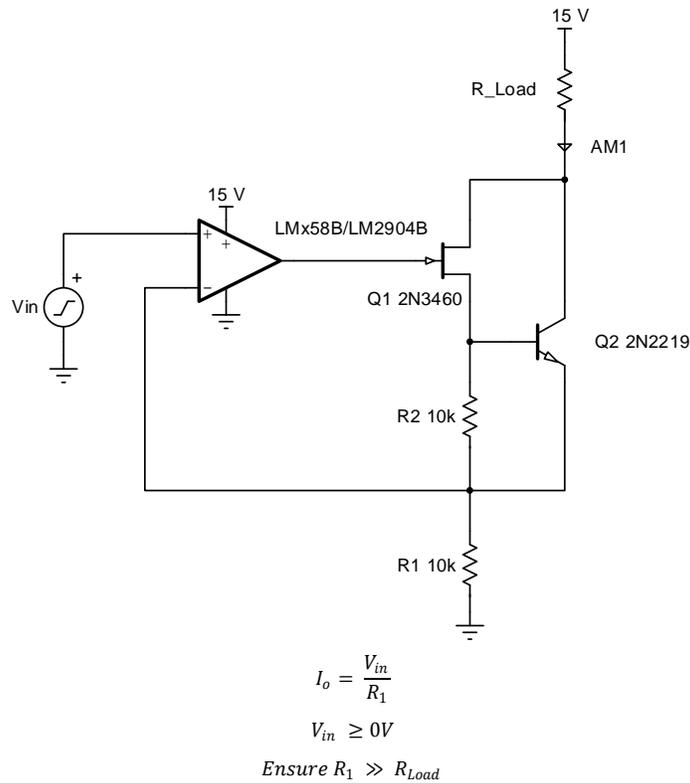


Figure 34. Current Sink

See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


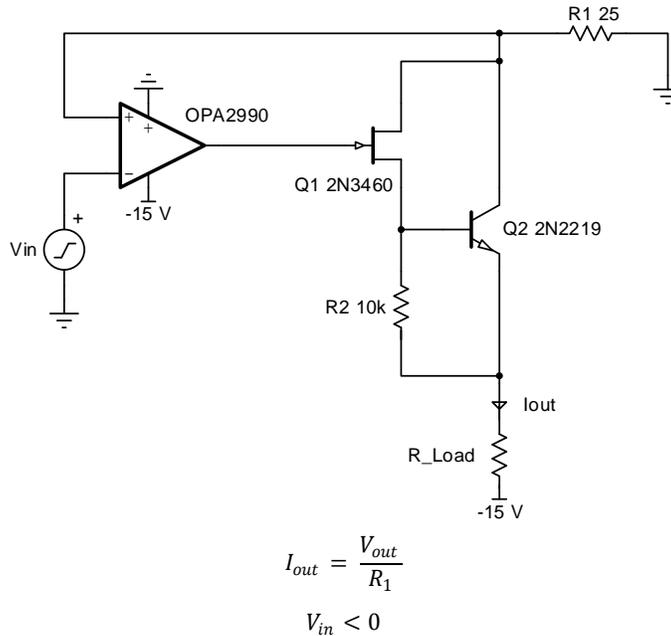


Figure 35. Current Source

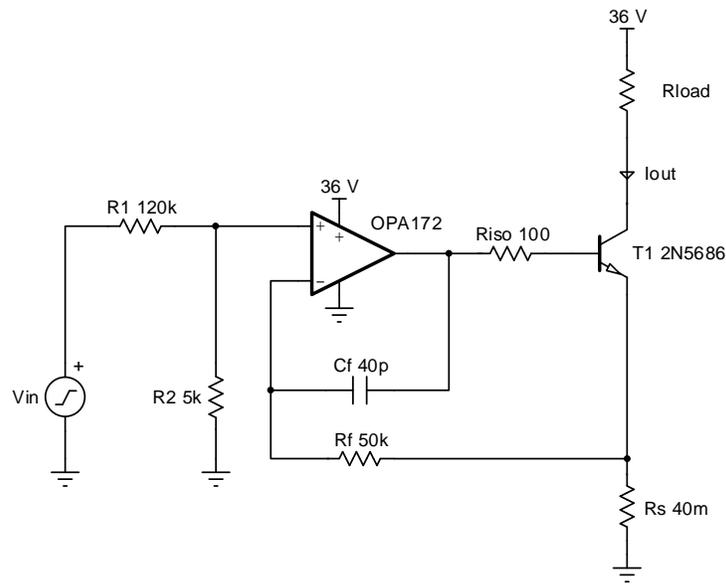See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = V_{in} \frac{R_2}{R_s(R_1 + R_2)}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

Figure 36. Voltage-to-Current Converter With BJT Output

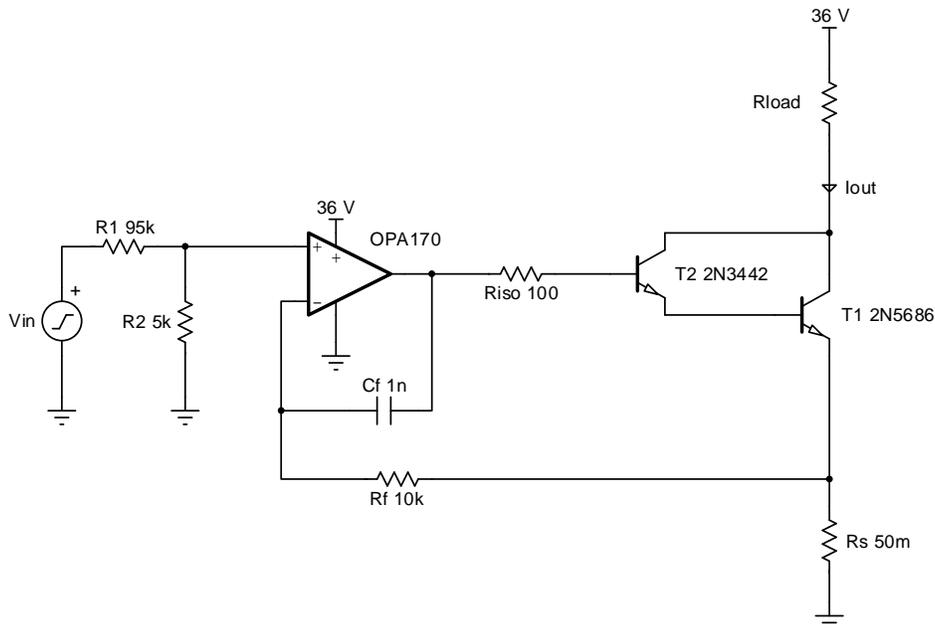Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = V_{in} \frac{R_2}{R_s(R_1 + R_2)}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

Figure 37. Voltage-to-Current Converter With Darlington Pair Output

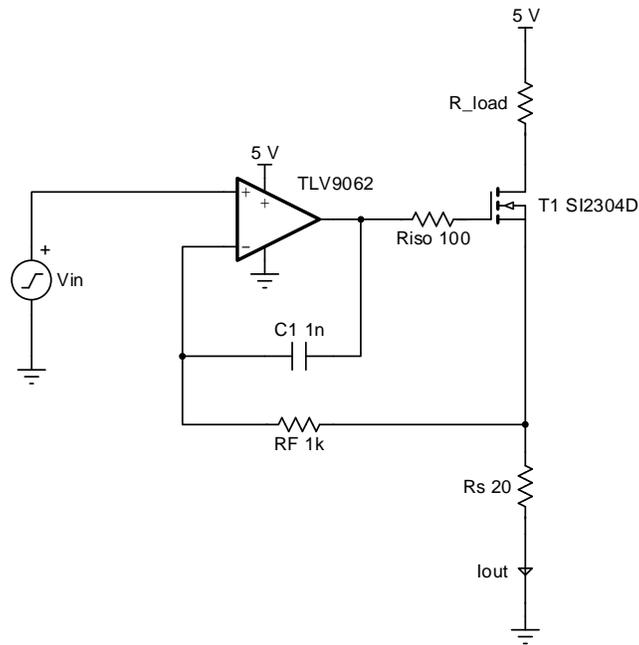Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = \frac{V_{in}}{R_s}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

Figure 38. Voltage-to-Current Converter With MOSFET Output

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

3 Signal Processing

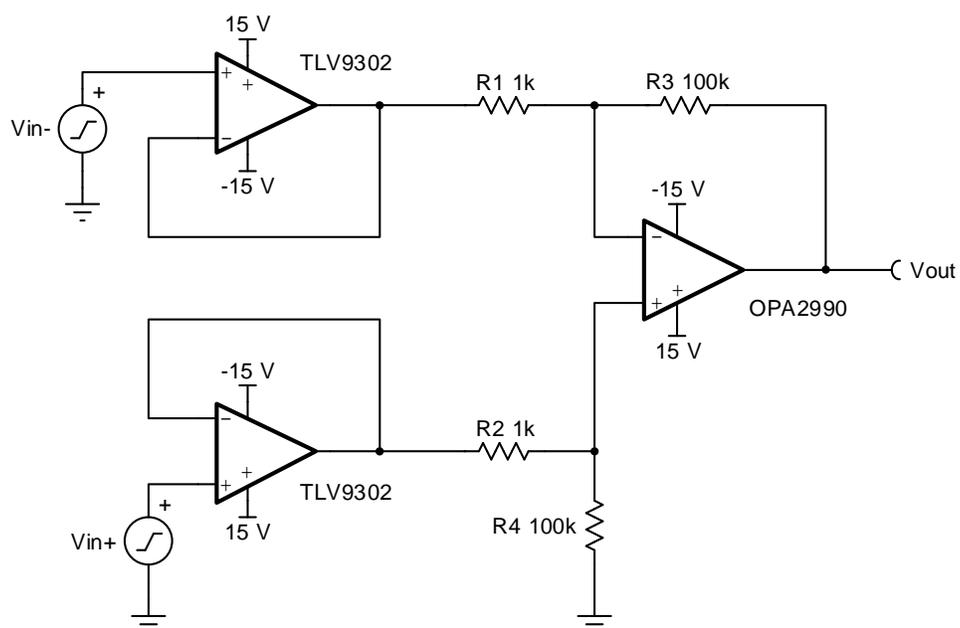


$$V_{out} = \frac{R_3}{R_1} (V_{in+} - V_{in-})$$

$$\frac{R_3}{R_1} = \frac{R_4}{R_2}$$

Figure 39. Instrumentation Amplifier

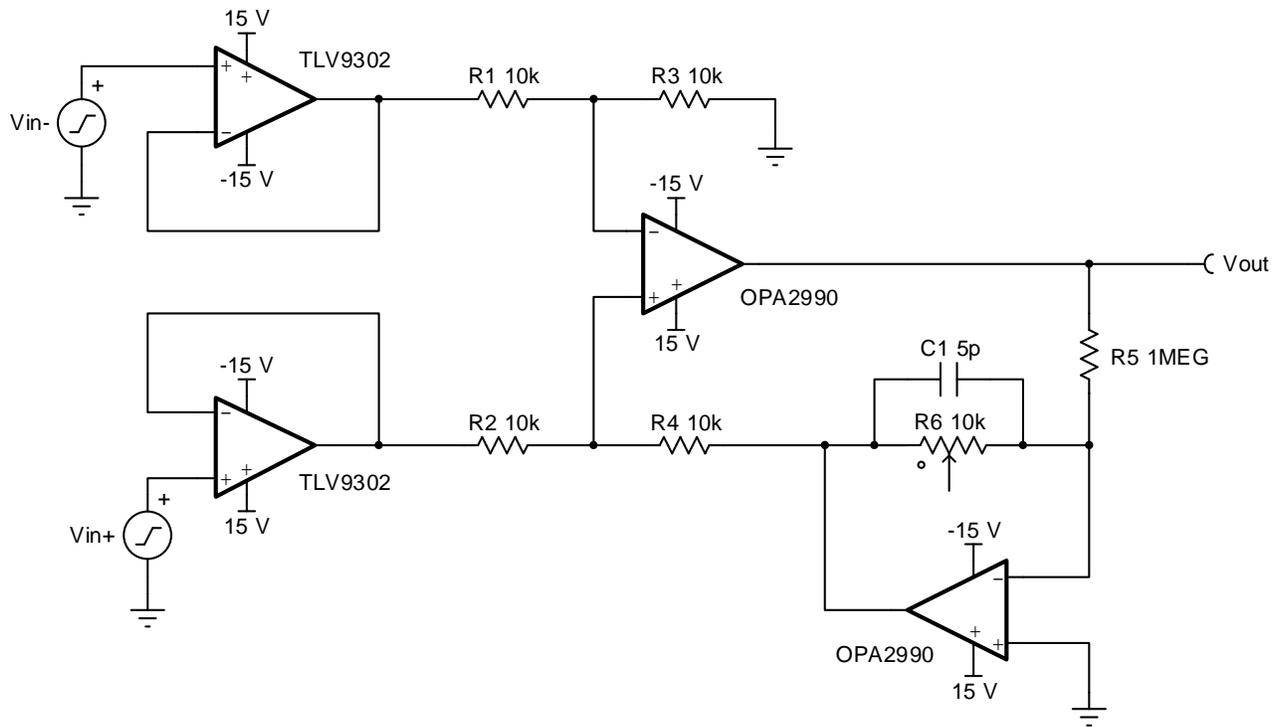Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \frac{10^{-4} R_6 R_3}{R_1} (V_{in+} - V_{in-})$$

$$\frac{R_3}{R_1} = \frac{R_4}{R_2}$$

Figure 40. Variable Gain Instrumentation Amplifier

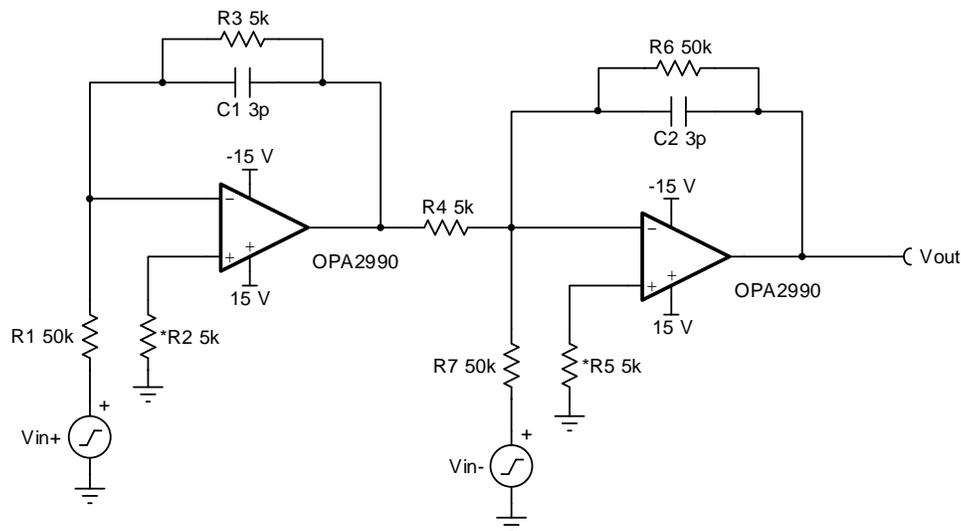Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = R_3 = R_4 = R_5$$


$$R_1 = R_6 = 10R_3$$

$$V_{out} = \left(\frac{R_7}{R_6}\right) V_{in}$$

* R_2 and R_5 Optional for Input Bias Current Cancellation

Figure 41. Instrumentation Amplifier With ± 100 -V Common Mode Range

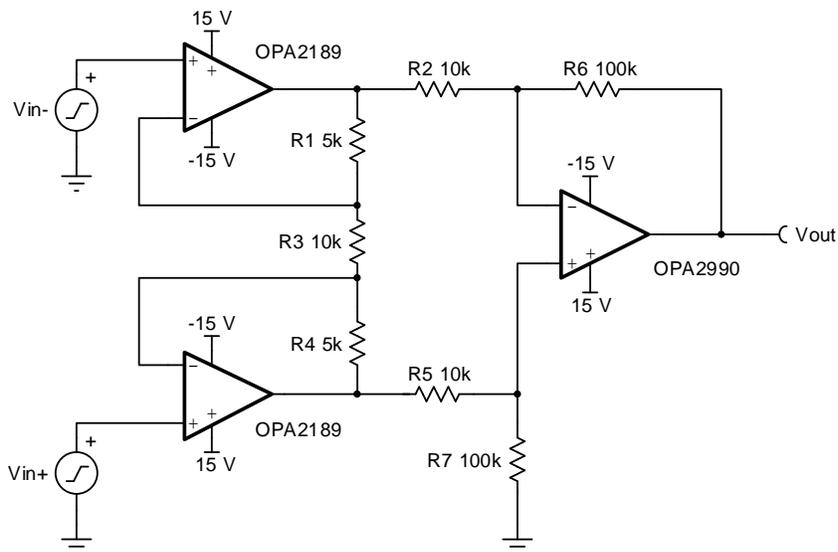Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_1 = R_4$$

$$R_2 = R_5$$

$$R_6 = R_7$$

$$V_{out} = \frac{R_6}{R_2} \left(1 + \frac{2R_1}{R_3}\right) V_{in}$$

Figure 42. Instrumentation Amplifier With ± 10 -V Common Mode Range

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

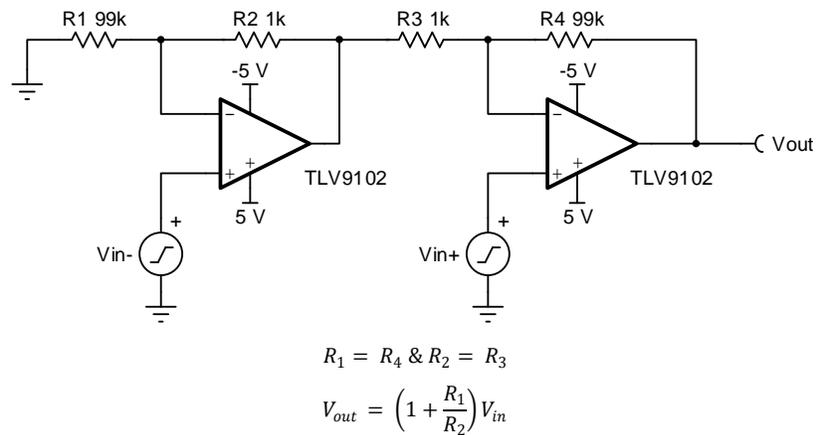


Figure 43. High Input Impedance Instrumentation Amplifier

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

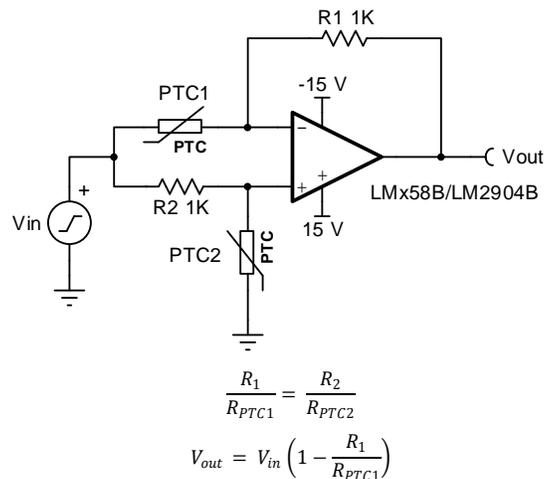


Figure 44. Bridge Amplifier With Temperature Sensitivity

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

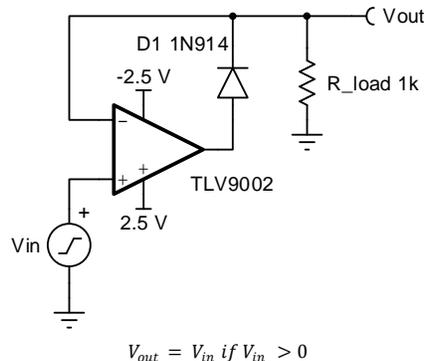


Figure 45. Precision Diode

For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


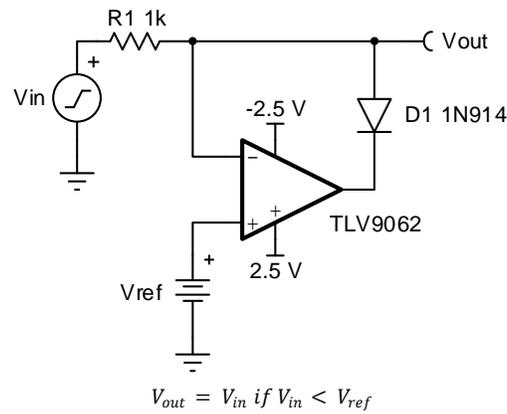


Figure 46. Precision Clamp

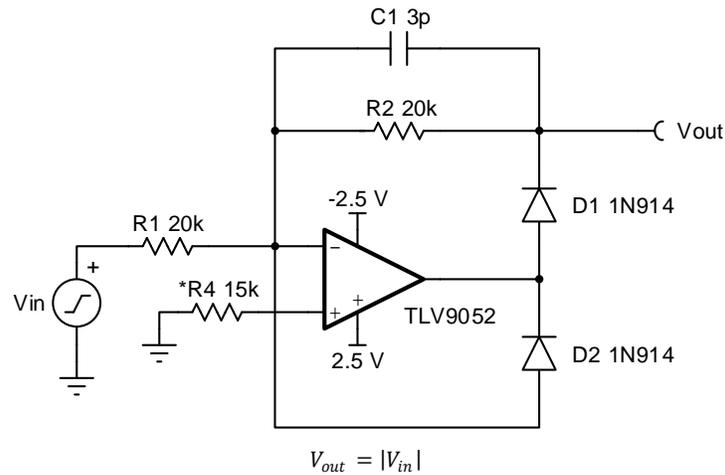
For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



* R_4 Optional for Input Bias Current Cancellation

Figure 47. Fast Half Wave Rectifier

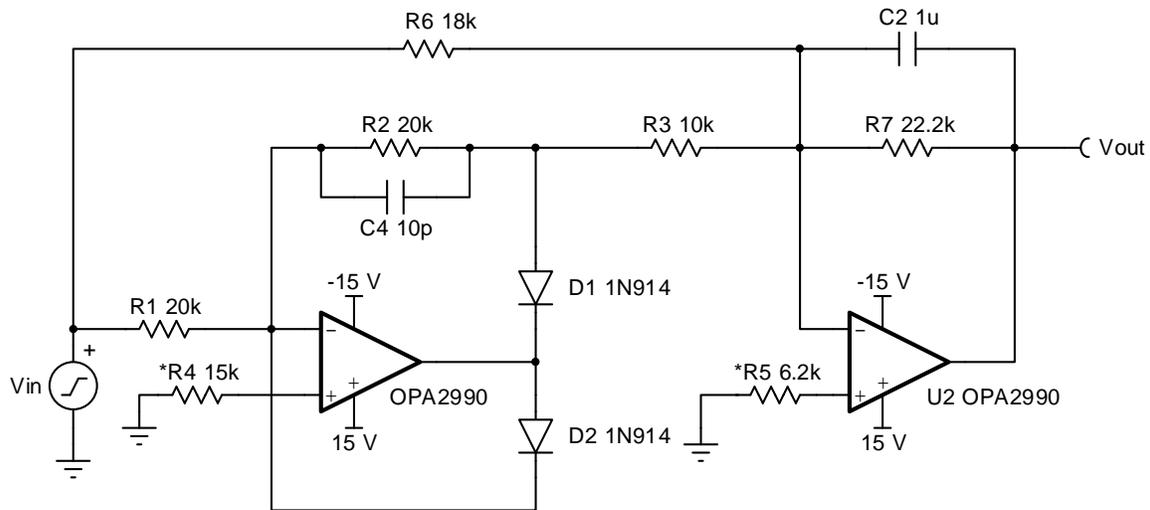For more information on this configuration, see [12]. See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = V_{in,avg}$$


$$0 < V_{in} < V_{cc} - V_{D1}$$

Ensure Op Amps Remain in Linear Range

* R₄ and R₅ Optional for Input Bias Current Cancellation

Figure 48. AC to DC Converter

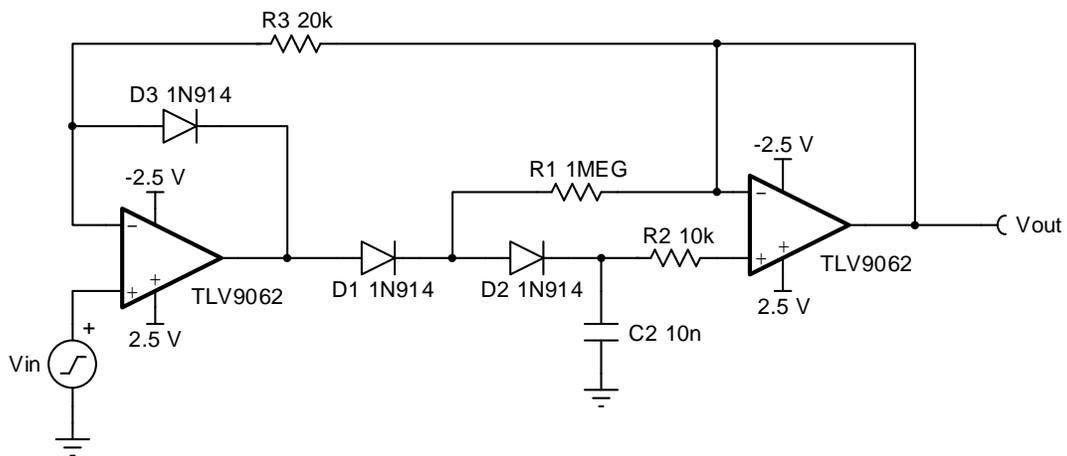
For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = V_{peak}$$

Figure 49. Peak Detector

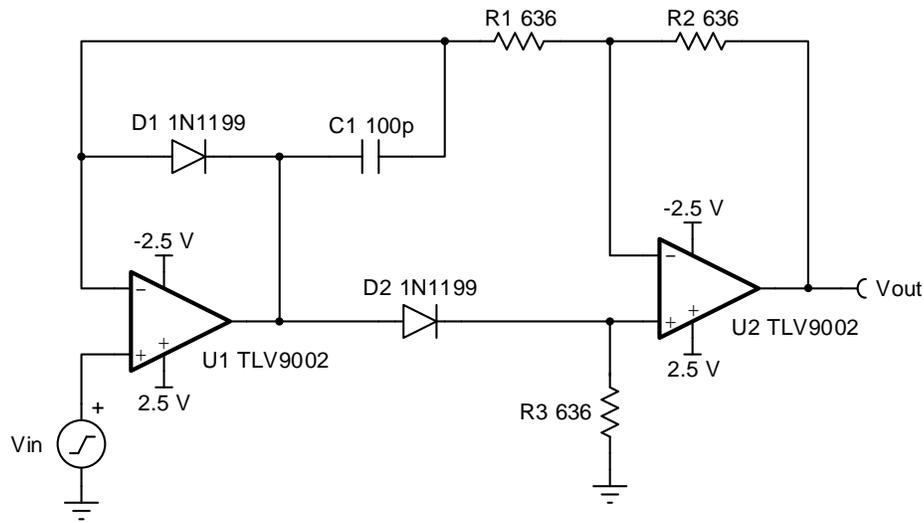Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = |V_{in}|$$

$$R_2 = R_1$$

$$\frac{GBW_{U2}}{4} = \frac{1}{2\pi R_1 C_1}$$

Figure 50. Absolute Value Amplifier

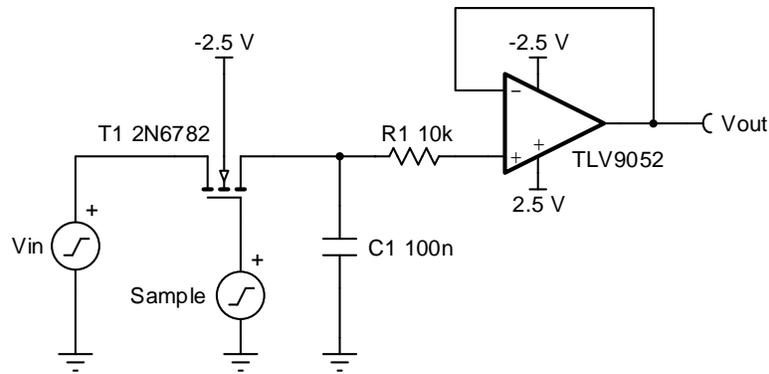For more information on this circuit, see [13]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$t_{sample} \propto C_1$$

$$Droop\ Rate \propto \frac{1}{C_1}$$

Figure 51. Sample and Hold I

For more information on this circuit, see [14]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


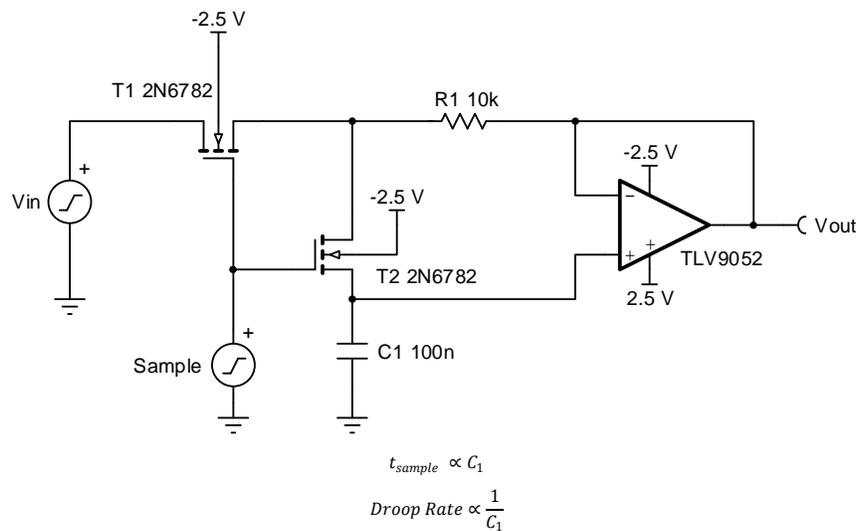


Figure 52. Sample and Hold II

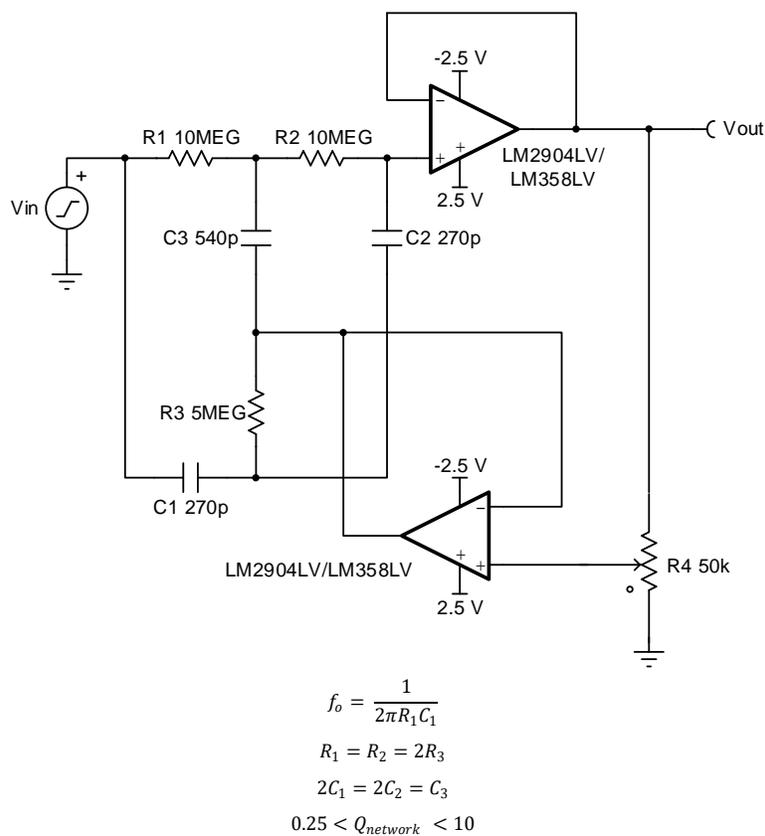
For more information on this circuit, see [14]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



Increasing Potentiometer Setting Increases $Q_{network}$

Figure 53. Adjustable Q Notch Filter

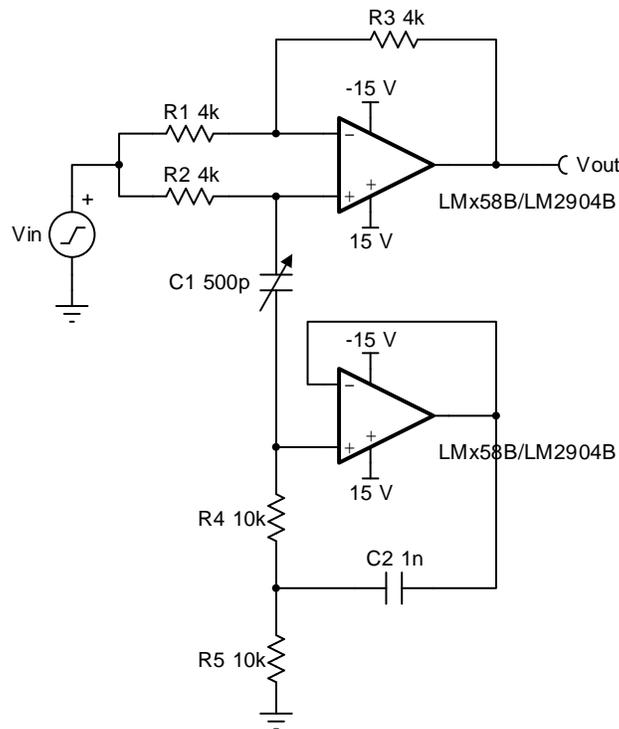For more information on this configuration, see [15] and [16]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$f_o = \frac{1}{2\pi R_4 \sqrt{C_1 C_2}}$$


$$R_4 = R_5$$

$$R_1 = R_3$$

$$R_4 = \frac{R_1}{2}$$

Figure 54. Easily Tuned Notch Filter

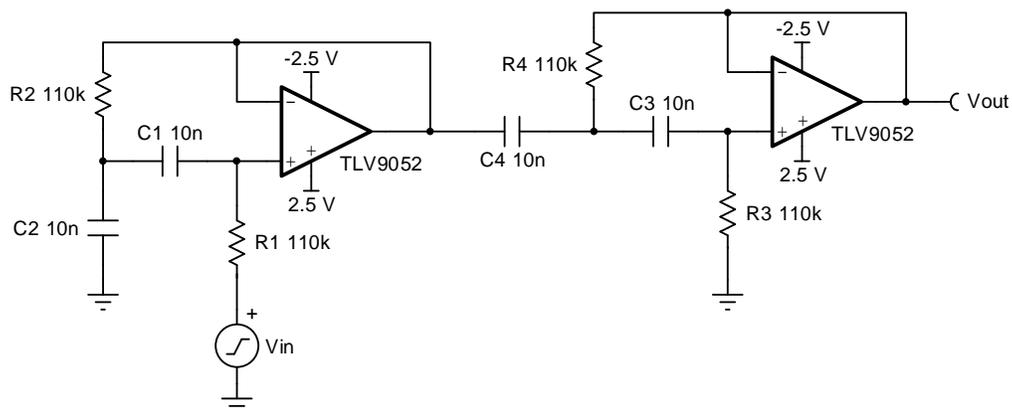For more information on this configuration, see [15] and [16]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$f_o = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

Figure 55. Sallen-Key Two-Stage Bandpass Filter

For more information on this configuration, see [17]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

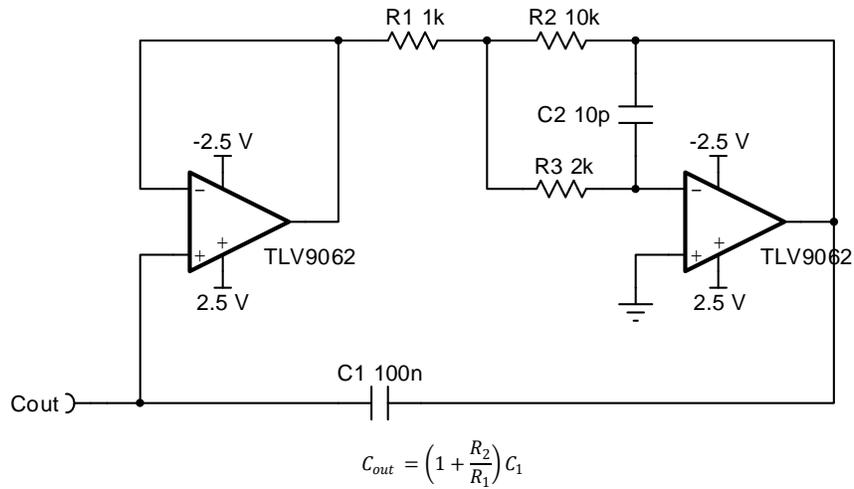


Figure 56. Two-Stage Capacitance Multiplier

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).


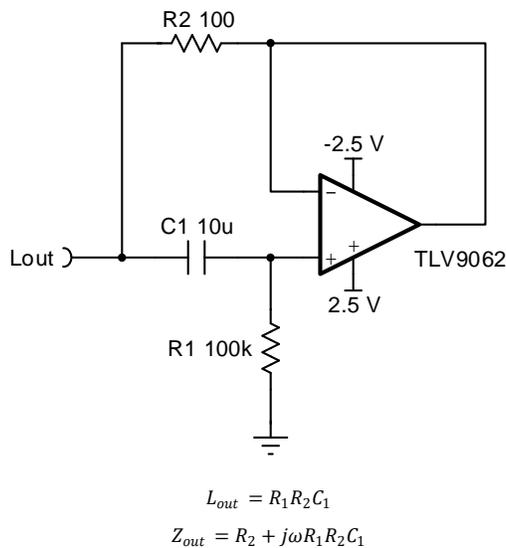


Figure 57. Simulated Inductor

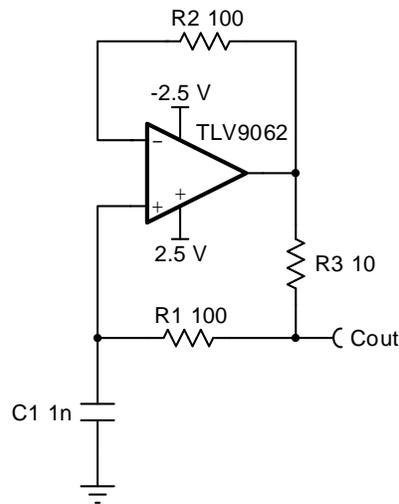For more information on this configuration, see [19]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$C_{out} \approx \frac{R_1}{R_3} C_1$$

$$C_1 \geq 100 \times C_{in \text{ amplifier}}$$

$$R_{source} \gg R_3$$

Figure 58. Capacitance Multiplier

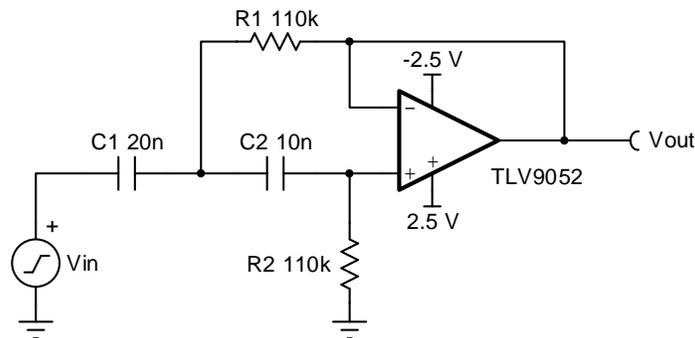Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = mR_1$$

$$C_2 = nC_1$$


$$f_c = \frac{1}{2\pi RC\sqrt{mn}}$$

$$Q = \frac{\sqrt{mn}}{m+1}$$

Choose m and n for desired f_c and Q

Figure 59. High Pass Sallen-Key Active Filter

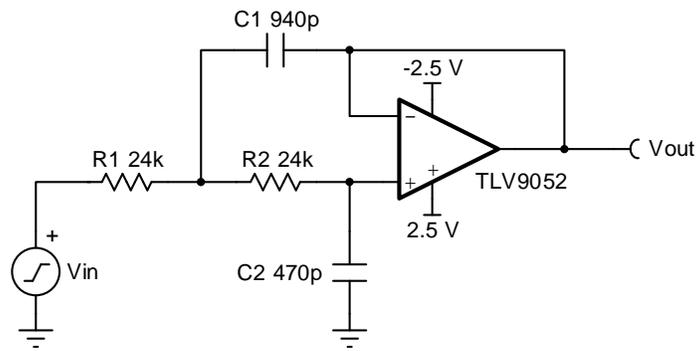For more information on this configuration, see [17]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_1 = mR_2$$

$$C_1 = nC_2$$


$$f_c = \frac{1}{2\pi RC\sqrt{mn}}$$

$$Q = \frac{\sqrt{mn}}{m+1}$$

Choose m and n for desired f_c and Q

Figure 60. Low Pass Sallen-Key Active Filter

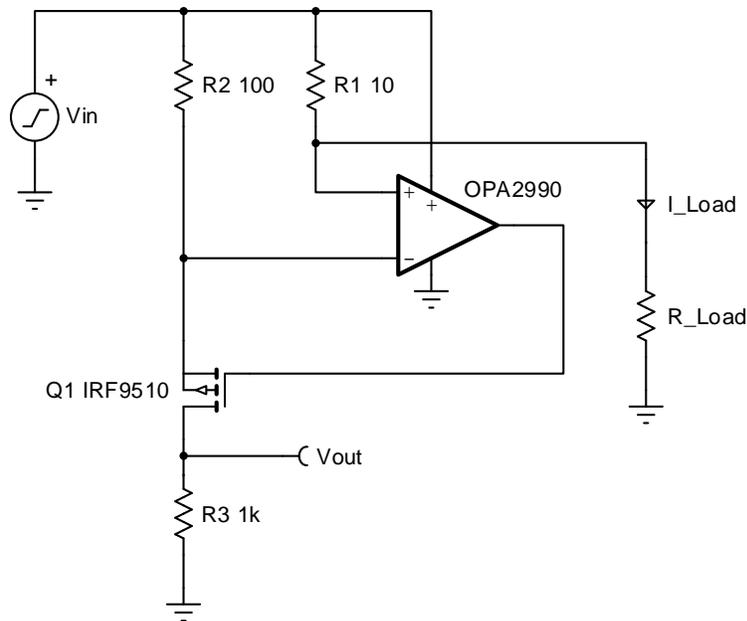
For more information on this configuration, see [17] and [18]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \frac{R_1 R_3}{R_2} I_L$$

Figure 61. Current Monitor

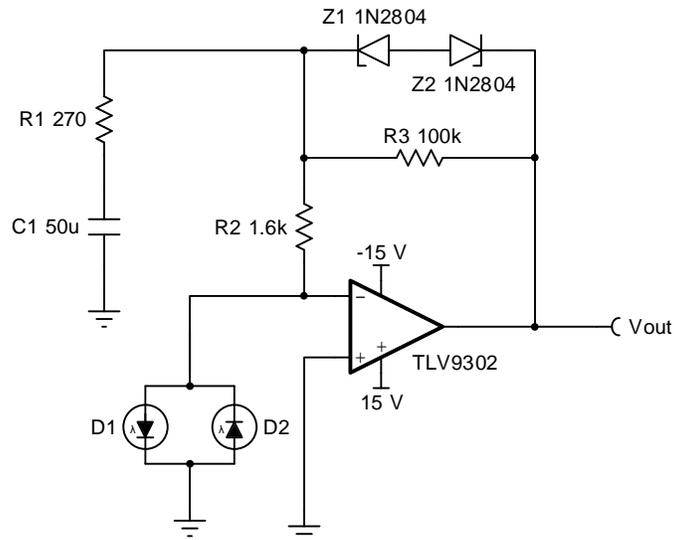Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \frac{0.1V}{\mu A} \text{ from } D1, D2$$

Linear Range through 60μA

Figure 62. Saturating Servo Preamplifier With Rate Feedback

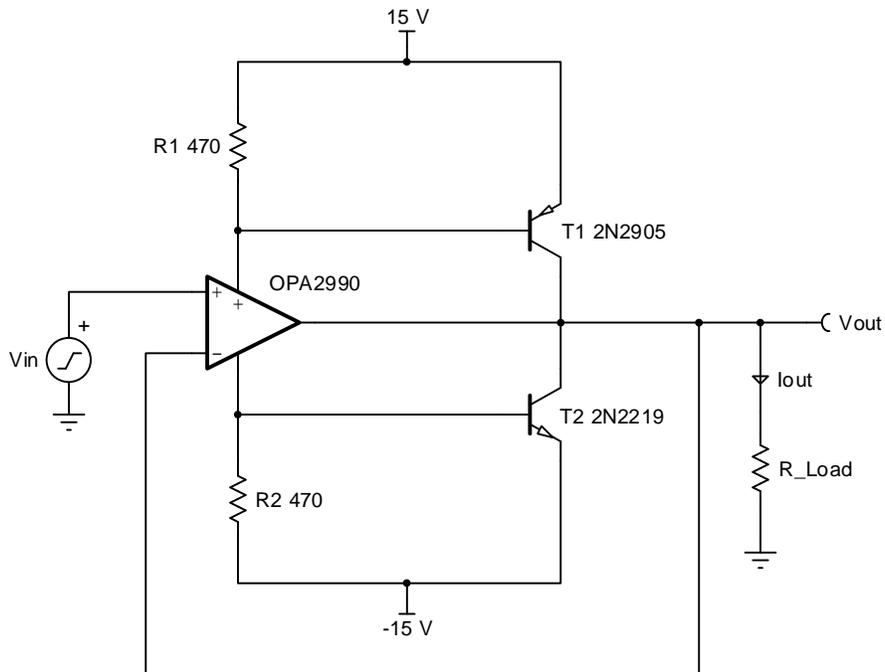For more information on modeling photodiodes, see [8]. More information on this configuration can be found in [20]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = V_{in}$$

Q_1 and Q_2 Increase I_{out}

Figure 63. Power Booster

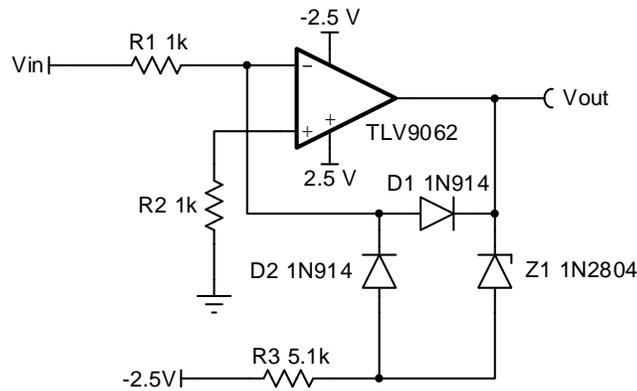
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



*Time to Detect Falling, Zero Crossing Reduced by ~65%
Versus Using Amplifier as Comparator*

Figure 64. Fast Zero Crossing Detector

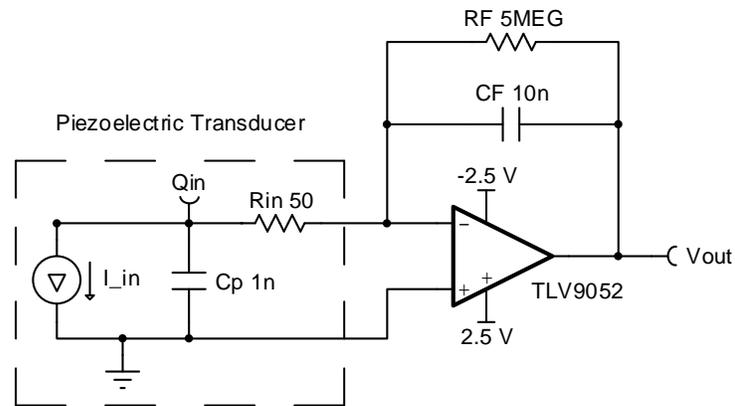Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$Gain = \frac{V_{out}}{Q_{in}} = \frac{1}{C_F}$$

$$f_{LPF} = \frac{1}{2\pi R_F C_F}$$

$$f_{HPF} = \frac{1}{2\pi R_{in} C_{in}}$$

Figure 65. Amplifier for Piezoelectric Transducer

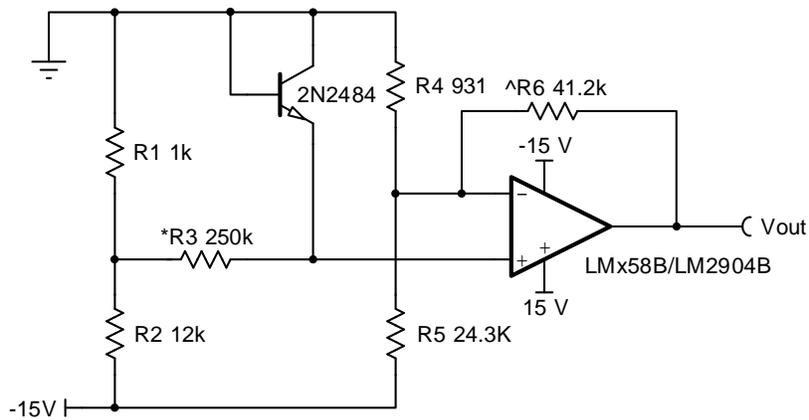For more information on this configuration, see [21] and [22]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = 103.9mV/^{\circ}C - 383mV$$

* Value Can Be Changed for 0V at 0°C

^Value Can Be Changed for 100mV/°C

Figure 66. Temperature Probe

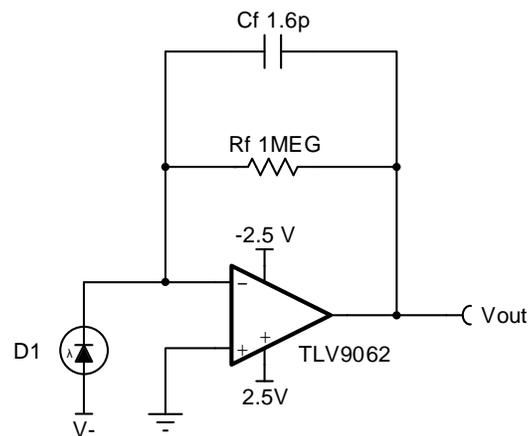
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = R_f I_D$$

Figure 67. Photodiode Amplifier I

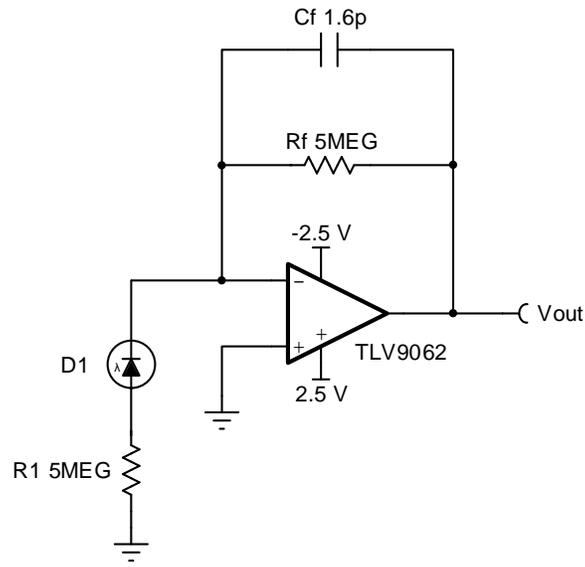
For more information on modeling photodiodes, see [8]. See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information on this circuit. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = 5V/\mu A \times \frac{R_f}{R_1}$$

Figure 68. Photodiode Amplifier II

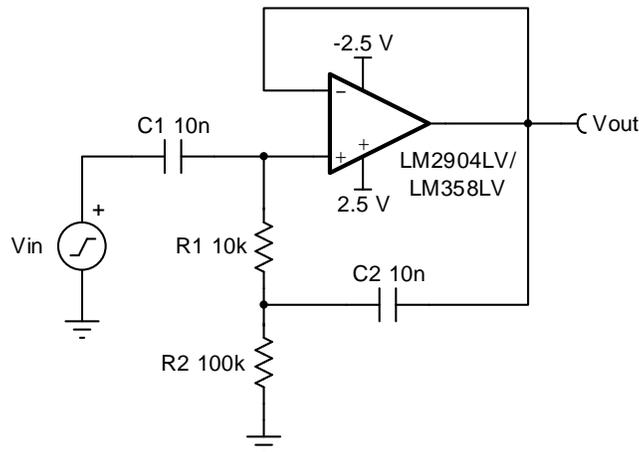
For more information on modeling photodiodes, see [8]. See [Analog engineer's circuit cookbook: amplifiers](#) for more information on this circuit. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \frac{(R_1 + R_2)C_1s + C_1C_2R_1R_2s^2}{1 + (R_1 + R_2)C_1s + C_1C_2R_1R_2s^2} V_{in}$$

Figure 69. High Input Impedance AC Follower

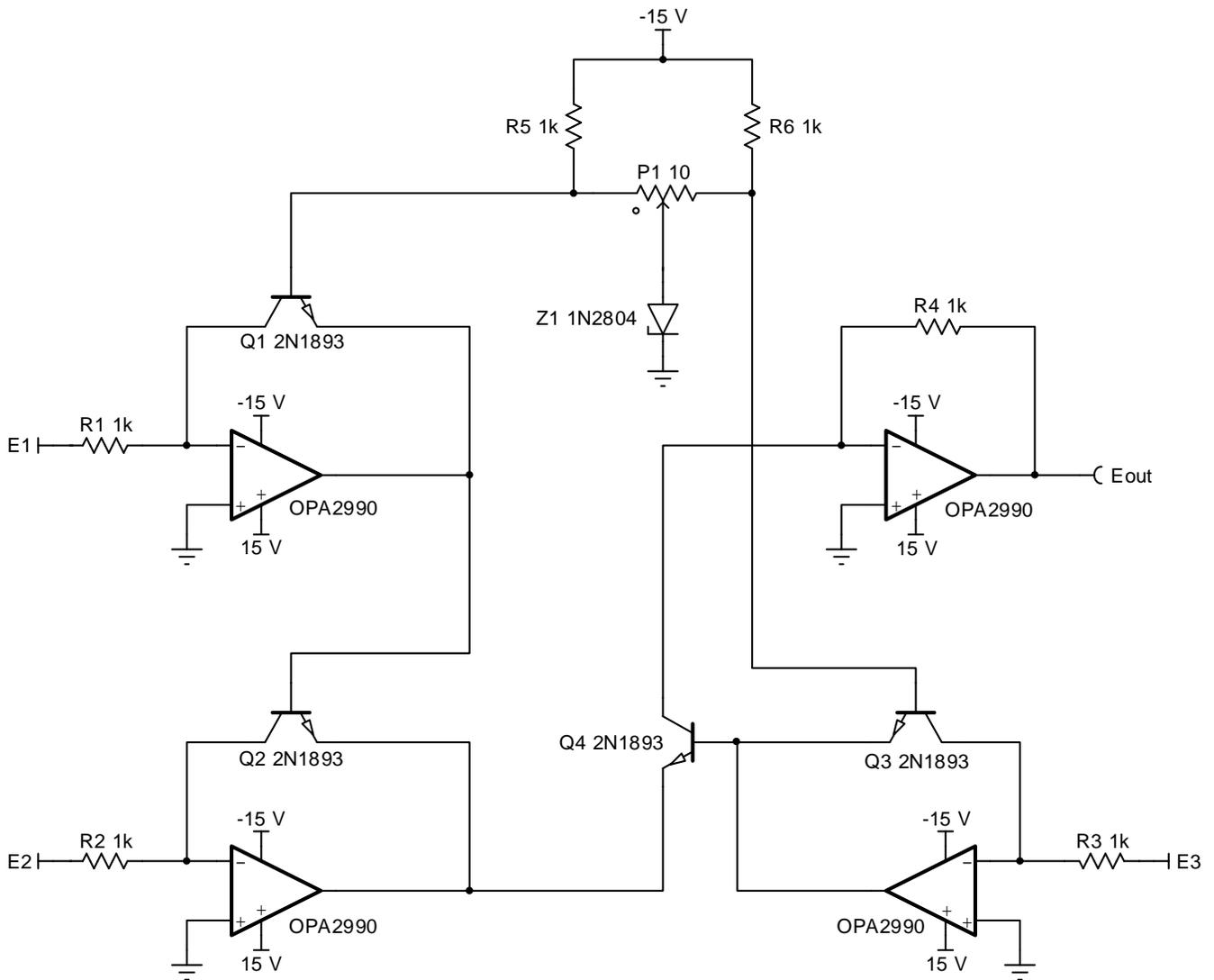Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$E_{out} = \frac{E_1 E_2}{E_3}$$

$$R_1 = R_2 = R_3 = R_4$$

Figure 70. Multiplier/Divider

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

4 References

1. To learn more about the design of many of these and other amplifier configurations, consult our [Analog engineer's circuit cookbook on amplifiers](#).
2. Alternatively, more information on several of these circuits can be found in our app note entitled, [AN-20 an applications guide for op amps](#).
3. To learn more about the characteristics of amplifiers, common techniques used in amplifier circuit design, and a variety of other amplifier topics, consult our [Texas Instruments Precision Labs video series on amplifiers](#).
4. For specific questions regarding your design, [reach out to our engineers via e2e](#), our online forum.
5. For a handy reference guide for your analog designs, check out the [Analog Engineer's Pocket Reference Guide](#) available for free in pdf form.
6. Use our [Analog Engineer's Calculator](#) to help crunch design equations.
7. Check out our [Amplifier's Product Page](#) to quickly sort through our products and find the amplifier(s) that best fit your needs.
8. For more information on modeling photodiodes including the model used in this design, see the [1 MHz, single-supply, photodiode amplifier reference design](#).
9. For more information on sine-wave oscillators, check out TI's app note on the [Sine-wave oscillator](#).
10. Alternatively, see our note on the [Design of op amp sine wave generators](#).
11. For more on the Howland Current Pump, see [AN-1515 a comprehensive study of the Howland current pump](#).
12. For more information on the Precision Diode, Precision Clamp, Half Wave Rectifier, and AC to DC Converter circuits, see our [LB-8 precision AC/DC converters](#) application note.
13. More information on the Absolute Value Amplifier can be found in our app note on [Precision absolute value circuits](#).
14. To learn more about Sample-and-Hold configurations, see our application note on the [Specifications and architectures of sample-and-hold amplifiers](#).
15. For more information on Q Notch Filters, see our [LB-5 high Q Notch filter](#) on the subject.
16. Further analysis of notch filters can be found in our app note on [High-speed notch filters](#).
17. For more information on Sallen-Key filter design, see our [Analysis of the Sallen-Key architecture](#) application note on the subject.
18. For more information on Low Pass Sallen-Key filter design, see our [Active low-pass filter design](#) application note.
19. More information on simulated inductors can be found in our application note entitled, [An audio circuit collection, part 3](#).
20. More information on a variety of circuits can be found in our [AN-4 monolithic op amp—the universal linear component](#) application note.
21. To learn more about the theory behind, design of, and simulation of piezoelectric transducers and their amplifiers, see this [Signal conditioning piezoelectric sensors](#) application note.
22. Additional information on piezoelectric transducers can be found in our analog applications journal entry, [Signal conditioning for piezoelectric sensors](#), on the subject.
23. For more information on the LM324/LM358 device family and how to properly connect unused inputs, see [Application design guidelines for LM324/LM358 devices](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated