


Sheet (1) - Electronics

Prof. Dr/ Essam Elshafee


1) A sample of germanium is doped to the extent of 10^{14} donor atoms/cm³ and 2×10^{14} acceptor atoms/cm³. At the temperature of the sample the conductivity of pure (intrinsic) germanium is $0.02 (\Omega\text{-cm})^{-1}$. If the total conduction current density is 0.128 A/cm^2 , find the applied electric field intensity. ($\mu_p = 1800 \text{ cm}^2/\text{V.s}$ and $\mu_n = 1800 \text{ cm}^2/\text{V.s}$ at 300°K).

2) What PIV rating is required for the diodes in a Full-Wave Center-Tapped Rectifier that produces an average output voltage of 60 V?

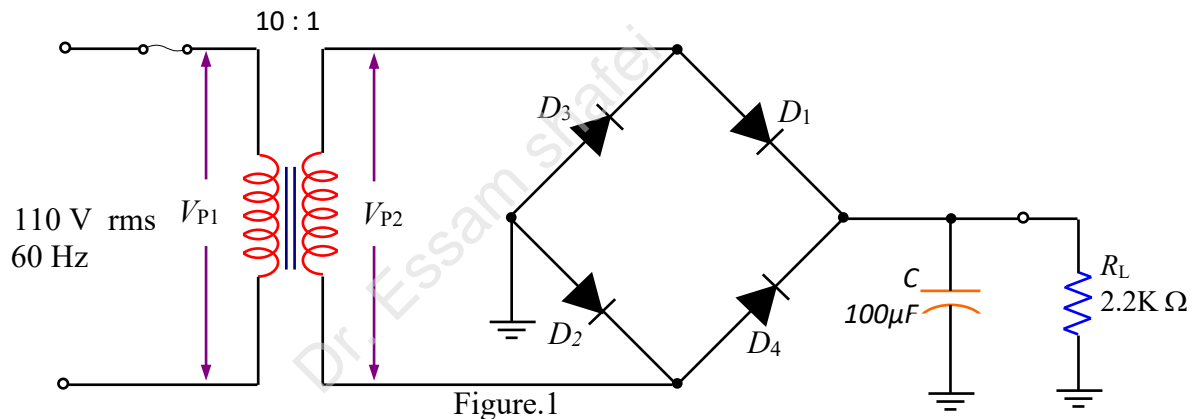3) Determine the ripple factor for the filtered rectifier with a load as indicated in Figure -1. What minimum PIV rating must the diodes have? ($V_\gamma = 0.7\text{V}$)



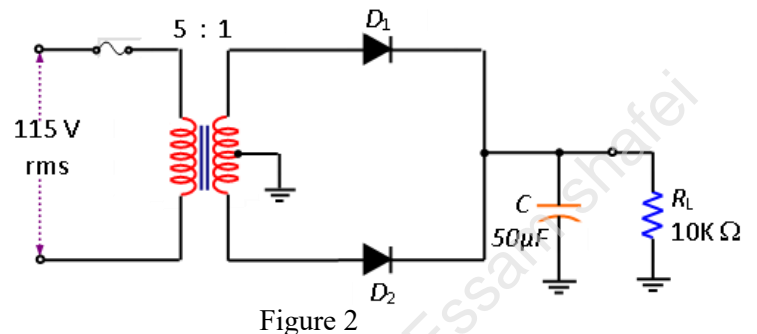4) Determine the ripple factor for the filtered rectifier with a load as indicated in Figure -2. What minimum PIV rating must the diodes have? ($V_\gamma = 0.7\text{V}$)




5) What value of filter capacitor is required to produce a 1% ripple factor for a full-wave rectifier having a load resistance of $1.5 \text{ k}\Omega$? Assume the rectifier produces a peak output of 18V from a 60 Hz ac source.


6) For the voltage regulator shown in Figure, assume that $V_Z=40V$, $R=40\Omega$, $r_Z=0$, and $R_L=400\Omega$. Voltage V_i varies between 48 and 60V.

(i) Specify the maximum and minimum current for the Zener diode.

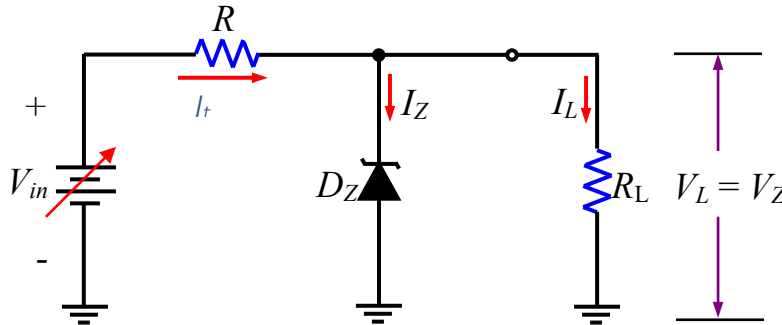(ii) Determine the maximum power dissipated in resistance R and in the zener diode ($P_{R(max)}$ and $P_{Z(max)}$).




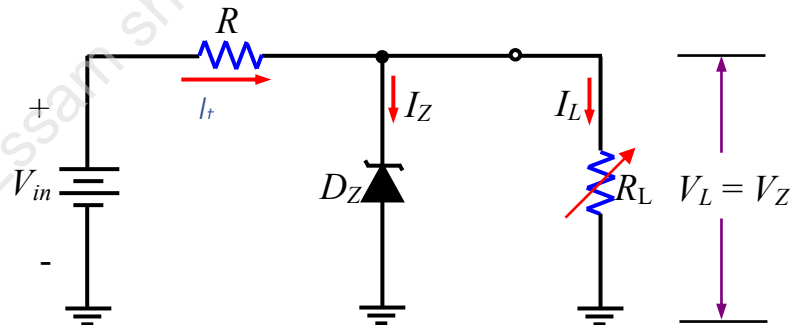7) For the voltage regulator shown in figure.2, assume that $V_Z=30V$, $V_{in}=150V$, $R=600\Omega$, $r_Z=0$, and $I_{ZK}=10\text{ mA}$, $I_{ZM}=190\text{ mA}$. Determine:
 (i) the variation in R_L over which the load voltage is still regulated at the Zener voltage.



(ii) the maximum power dissipated in resistance R_L and in the Zener diode ($P_{L(max)}$ and $P_{Z(max)}$)

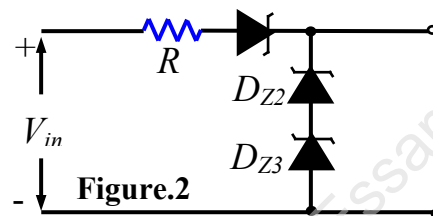
8) For the circuit shown in Figure-2 $I_{o1}=2\mu A$, $I_{o2}=1\mu A$, $I_{o3}=3\mu A$, $V_{Z1}=20V$, $V_{Z2}=30V$, $V_{Z3}=50V$, $r_{Z1}=10\Omega$, $r_{Z2}=30\Omega$, $r_{Z3}=20\Omega$, $V_{\gamma1}=V_{\gamma2}=0.6V$, $V_{\gamma3}=0.5V$, and $R=10k\Omega$. Calculate the current passing through the circuit if $V_{in} = -10V$, $V_{in} = +10V$, $V_{in} = -60V$ and $V_{in} = 60V$.




Sheet (2) – Electronics (1)

Prof. Dr/ Essam Elshafi

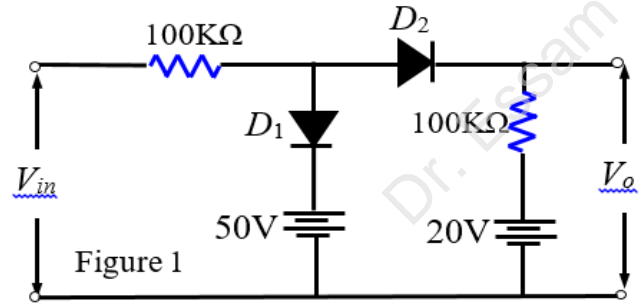
- 1) The diodes shown in Figure.1 are ideal. Sketch the transfer characteristics for $0 \leq V_i \leq 100V$. Indicate the state of each diode (on or off) over each region of the characteristic.



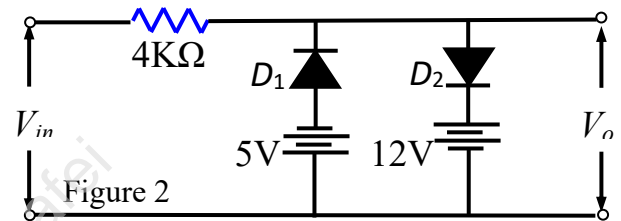
- 2) The diodes shown in Figure.2 are ideal. Sketch the transfer characteristics for $-20 \leq V_i \leq 20V$. Indicate the state of each diode (on or off) over each region of the characteristic.



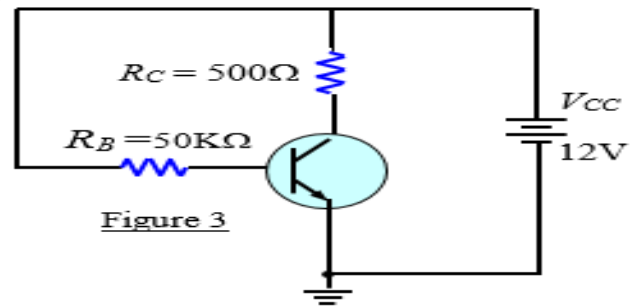
- 3) Determine whether or not the transistor shown in Figure 3 is in saturation. Assume $V_{CE(sat.)} = 0.2 V$ and $\beta = 150$.



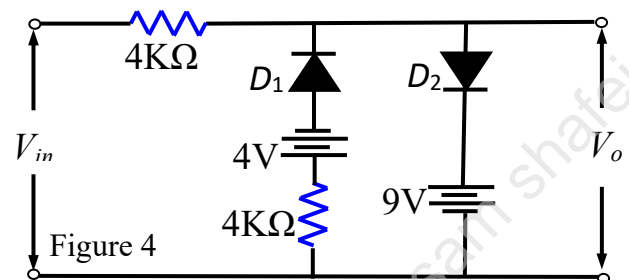- 4) The diodes shown in Figure.4 are ideal. Sketch the transfer characteristics for $-20 \leq V_i \leq 20V$. Indicate the state of each diode (on or off) over each region of the characteristic.



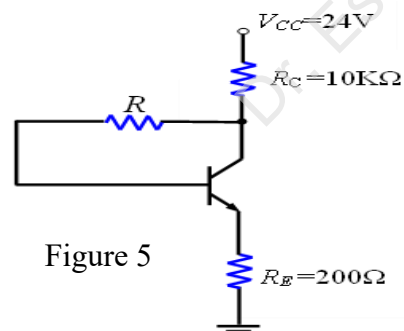- 5) If $\beta = 45$, $I_E = 2mA$ and $V_{BE} = 0.7V$, find R in the circuit shown in figure.5



- 6) If $\beta = 45$ and $V_{BE} = 0.7V$, find R in the amplifier circuit shown in Figure.6 for a zener current $I_Z = 2mA$.

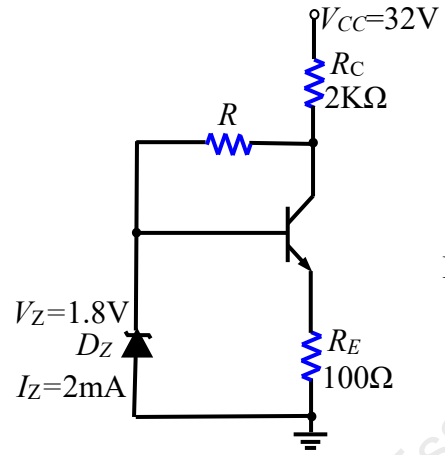


Figure 6

- 7) If $\beta = 49$ and $V_{BE} = 0.7V$, find R in the circuit shown in figure.7 for an collector current $I_C = 1.96mA$.

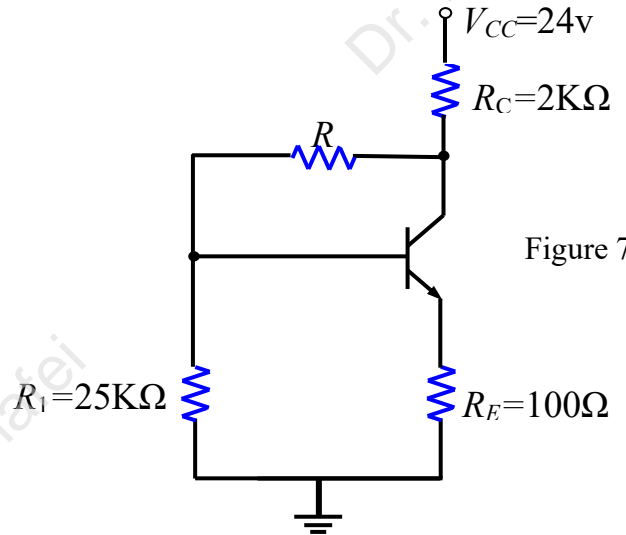


Figure 7

- 8) For each transistor in the circuit shown in Figure.8, the parameters are $\beta = 100$, and $V_{BE} = 0.7V$. Determine the quiescent base, collector, and emitter currents in Q_1 and Q_2 , Also determine V_{CEQ1} and V_{CEQ2}

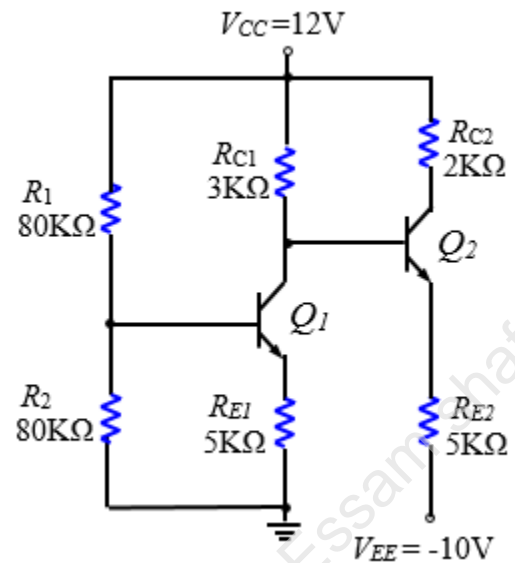


Figure 8